



## Lecture 2: Switches, Rectifiers and Generators

### Topics:


- 1) Homework Review
- 2) Switches
- 3) Bridge Rectifiers
- 4) AC vs. DC
- 5) Function Generators and Oscilloscopes

### Homework Review:

#### Homework 1: Voltage dividers

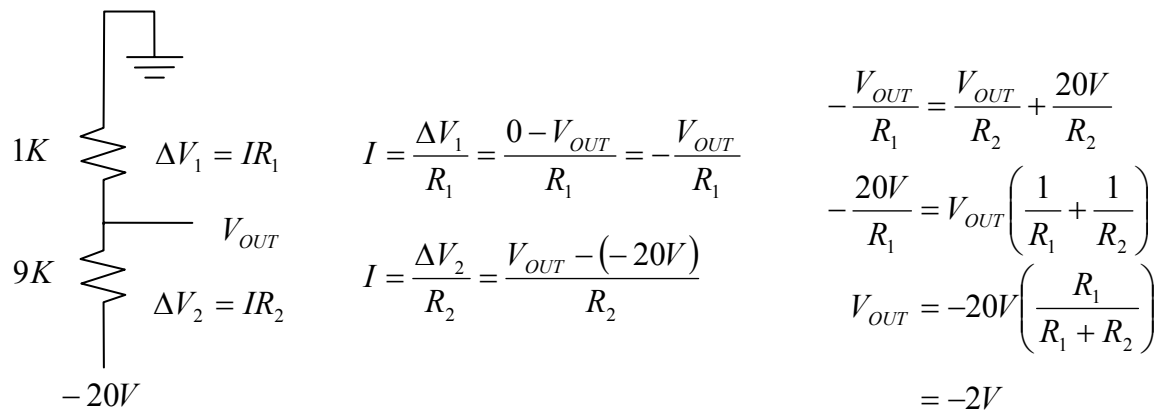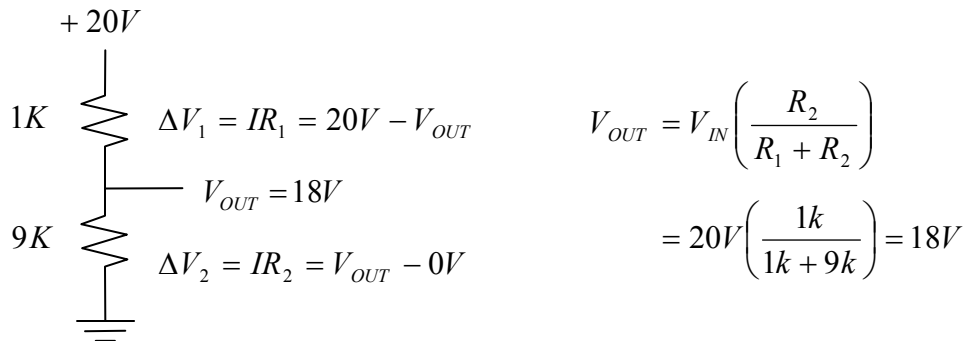

## Homework 2: Diodes

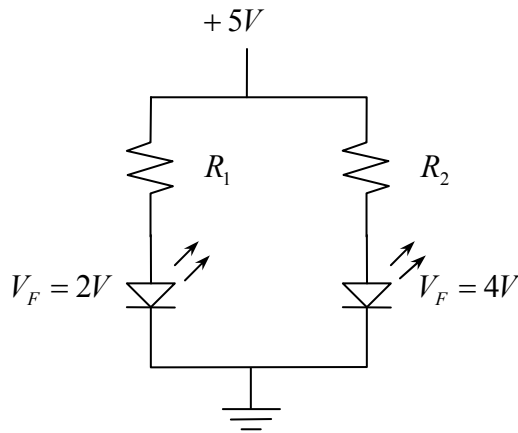


$$R_1 = \frac{(5V - 2V)}{20mA} = 150\Omega$$

$$R_2 = \frac{(5V - 4V)}{20mA} = 50\Omega$$


There are two diodes that will be used in class:

- Zener diodes: If you put a negative voltage across a Zener diode, it has a second turn-on point. The slope of the I-V curve of the second turn-on point is even more abrupt than the slope of the I-V curve of the first turn-on point. You can tailor the breakdown voltage from a couple of volts to hundreds of volts. A Zener diode is used in reverse bias to clamp and hold the voltage. The name Zener diode comes from a Physics term called the Zener effect, which is not even related to the Zener diode at all. However, the Zener diode does exhibit the Avalanche effect.
- Silicon diodes: These diodes do not emit light. Have same functionality as other diodes. Their forward voltages are really small ( $\sim 0.6$ - $0.7$  volts).

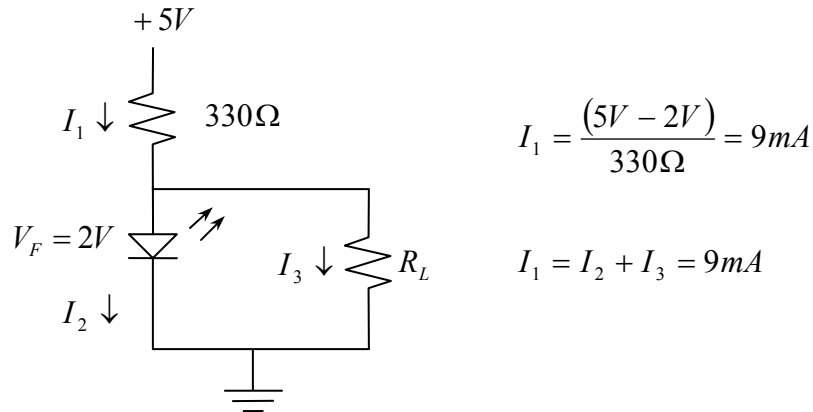Diodes don't have resistance. If the voltage is below a diode's forward voltage, then the element looks like an open circuit. If the voltage is above the forward voltage, the element behaves as a short circuit.



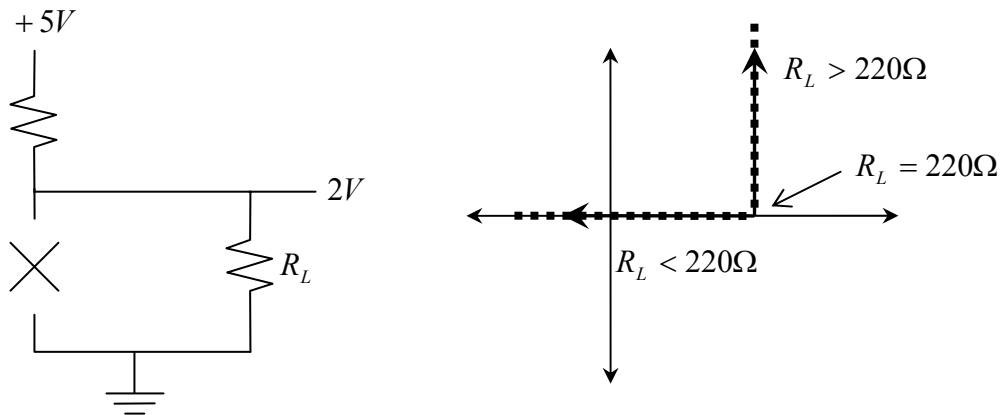If  $R_L$  is such that  $V_{OUT} = 1V$ , there is no current flow through the diode. The diode conducts (turns on) when  $V_{OUT}$  hits  $R_L$ .




One gets  $V_{OUT} = 2V$  when  $R_L = 220$  ohms.

Now, try  $R_L = 330$  ohms. The voltage divider predicts  $V_{OUT} = 2.5V$ . BUT the diode clamps at 2.0V! The diode will steal any necessary current to stay at 2V. The bigger  $R_L$  is, the more current passes through the diode.
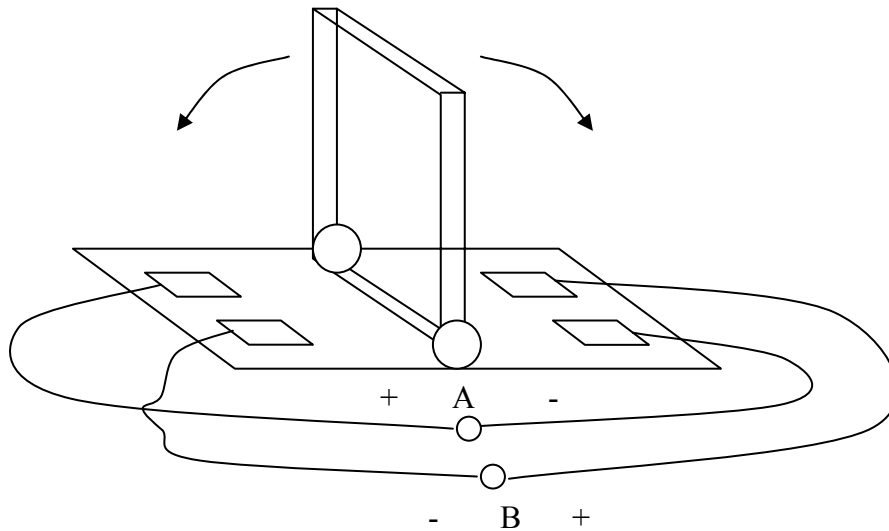
## AC vs. DC

One can implement a simple DC to AC converter with a switch configuration like the following:



With switch to one position:

$$V_A - V_B = 9V$$

With switch on the other position:

$$V_B - V_A = -9V$$

