
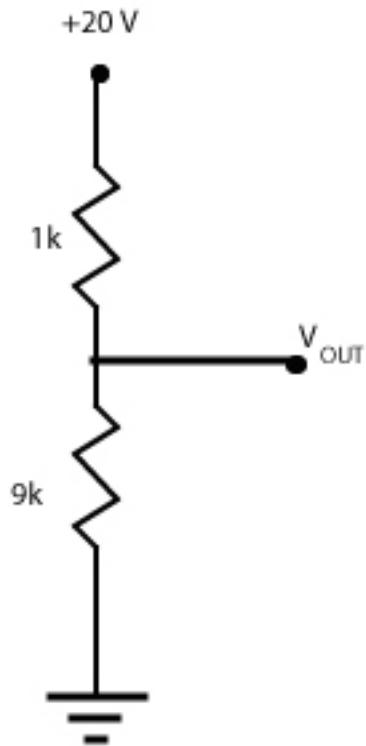



SP.764 Fall 04 - Problem Set 1

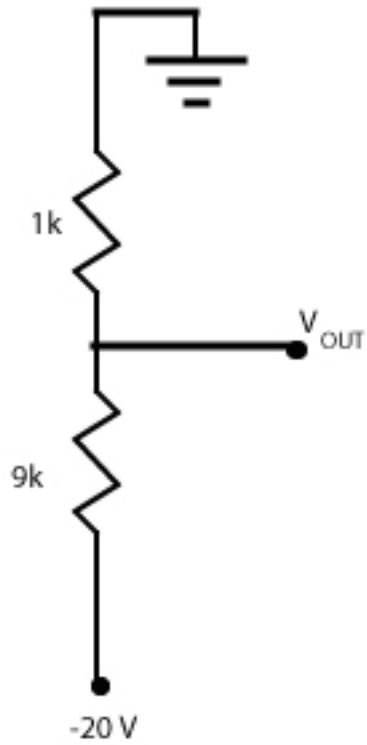

Circuit A



Circuit B

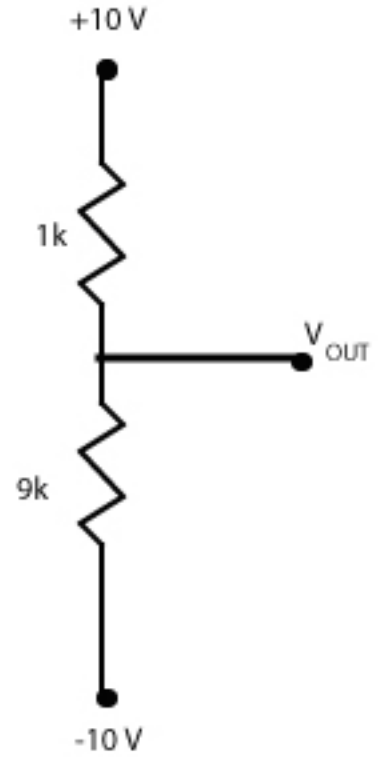

Circuit C

Calculate V_{OUT} for each circuit above. Please show your calculation.

Note: The voltage divider equation derived in class doesn't work for circuits B & C.