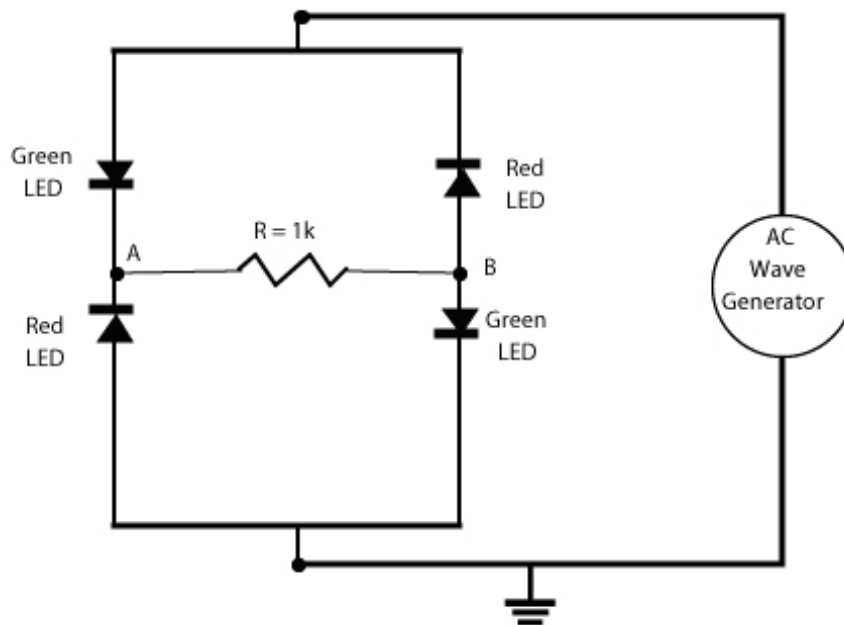


SP.764 Fall 04 - Problem Set 3



Assume that the red LED turns on with a forward voltage of 1.5 V, and that the green LED turns on with a forward voltage of 2.0 V.

1. Sketch a plot of 2 cycles of a ± 5 V square wave from the AC wave generator.
2. Sketch a plot of the voltage measured between points A and Ground below your plot from Q. 1
3. Sketch a plot of the voltage measured between points B and Ground below your plot from Q. 1
4. Sketch a plot of the voltage measured between points A and B below your plot from Q. 1
5. Repeat Q.'s 1 through 4 for a sine wave