

AERO | ASTRO



# 16.682 - Prototyping Avionics Spring 2006

LECTURE 4

February 21, 2006

DEPARTMENT OF AERONAUTICS AND ASTRONAUTICS


**Alvar Saenz-Otero**

# Outline

- **Amplifiers**
  - **Ideal vs. Real**
  - **Basic linear uses**
    - **Voltage follower (current source)**
    - **Voltage amplifier**
    - **Voltage invert & subtract**
  - **Positive feedback**
  - **Active filters**

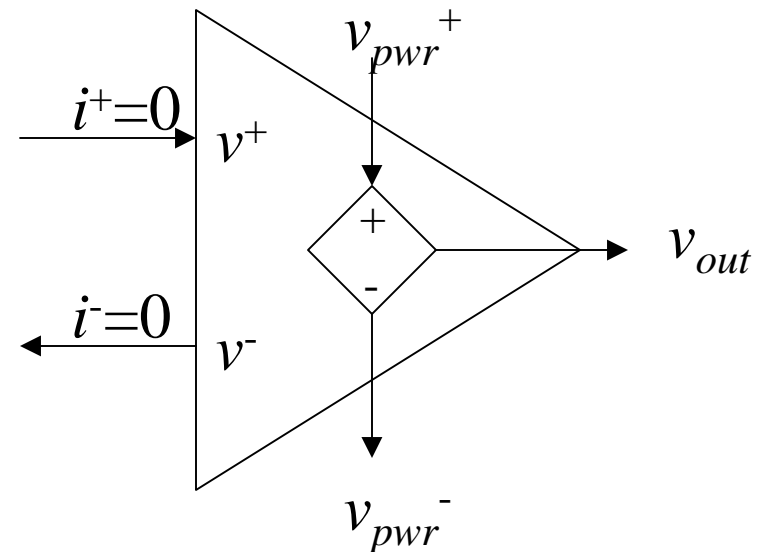
# Operational Amplifiers

- Assume ideal during development:
  - $v^+ = v^-$
  - $i^+ = 0, i^- = 0$
  - Saturation at input power voltage only
  - Linear
- Keep in mind for implementation:
  - Maximum amplification (e.g., 100, 1000, normally max  $< 10^6$ )
  - Saturation
    - Op-Amps require external +/- supplies!
  - Non-linear region
    - Frequency region



# OpAmp Examples

- Buffer/follower

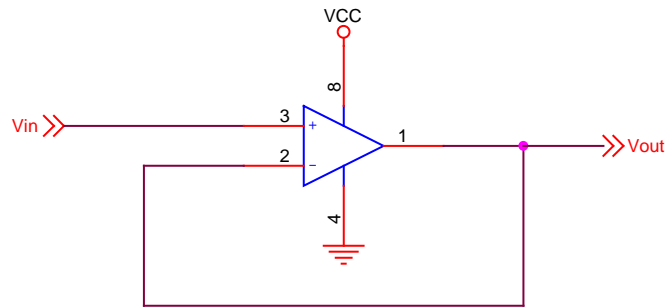


$$v^+ = v^-$$

$$v^+ = V_{in}$$

$$v^- = V_{out}$$

$$V_{out} = V_{in}$$

- Amplifier

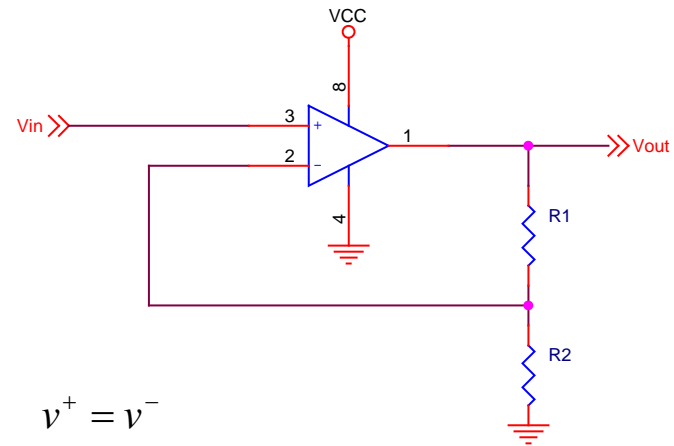

$$v^+ = v^-$$

$$v^+ = V_{in}$$


$$i^- = 0 \rightarrow i_R = \frac{V_{out}}{R_1 + R_2}$$

$$v^- = R_2 \frac{V_{out}}{R_1 + R_2} = v^+ = V_{in}$$

$$V_{out} = V_{in} \frac{R_1 + R_2}{R_2}$$


# OpAmp Examples

- Buffer/follower

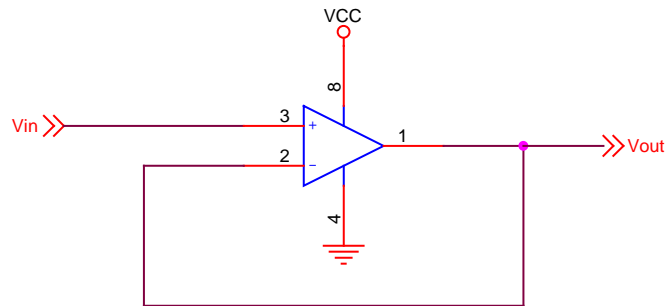

$$\begin{aligned}v^+ &= v^- \\v^+ &= V_{in} \\v^- &= V_{out} \\V_{out} &= V_{in}\end{aligned}$$


- Amplifier

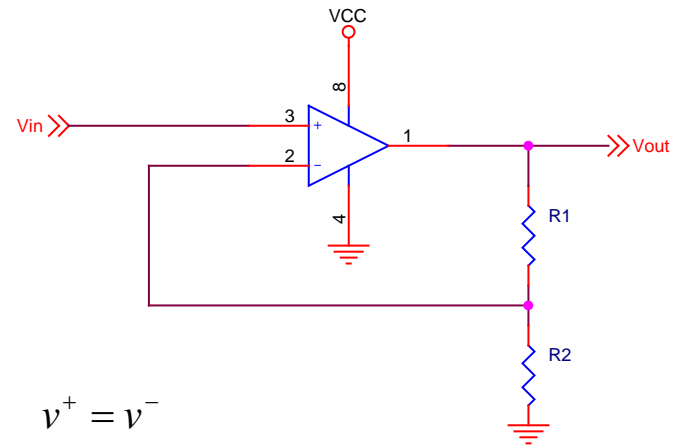

$$\begin{aligned}v^+ &= v^- \\v^+ &= V_{in} \\i^- &= 0 \rightarrow i_R = \frac{V_{out}}{R_1 + R_2} \\v^- &= R_2 \frac{V_{out}}{R_1 + R_2} = v^+ = V_{in} \\V_{out} &= V_{in} \frac{R_1 + R_2}{R_2}\end{aligned}$$

# OpAmp Examples

- Inverting Amplifier**

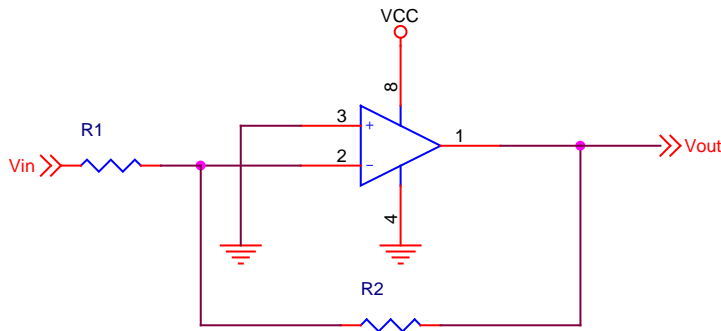


$$v^+ = v^- = 0$$

$$i^- = 0 \rightarrow i_R = \frac{V_{in}}{R_1}$$

$$V_{out} = -i_R \cdot R_2 = -V_{in} \frac{R_2}{R_1}$$

- Amplifier/subtract**

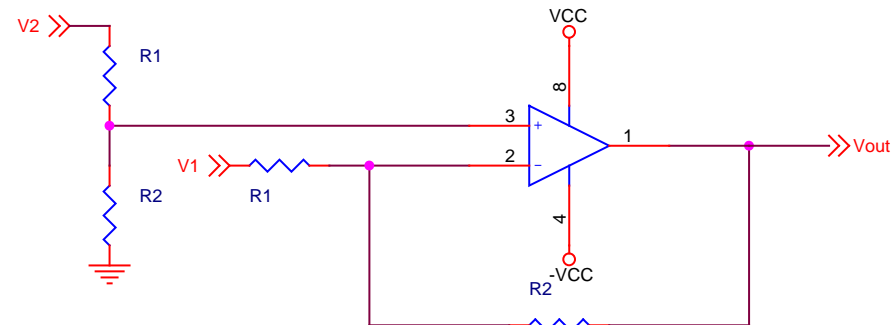

$$v^+ = v^-$$

$$v^+ = V_2 \frac{R_2}{R_1 + R_2}$$


$$v^- = V_{out} + R_2 \frac{V_1 - V_{out}}{R_1 + R_2}$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

**But these do NOT work when  $V_{in} > 0$ . Why? ...**

# OpAmp Examples

- Inverting Amplifier**

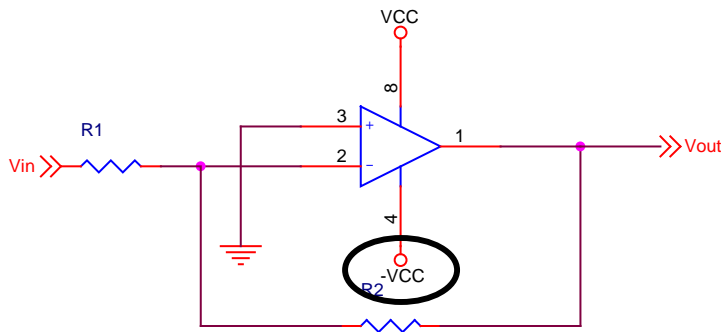


$$v^+ = v^- = 0$$

$$i^- = 0 \rightarrow i_R = \frac{V_{in}}{R_1}$$

$$V_{out} = -i_R \cdot R_2 = -V_{in} \frac{R_2}{R_1}$$

- Amplifier/subtract**

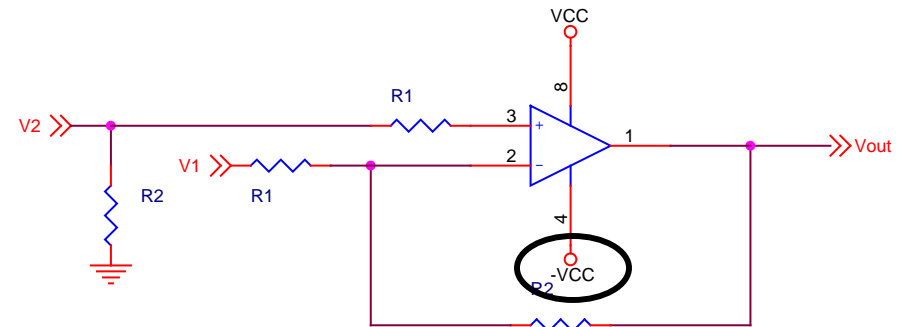

$$v^+ = v^-$$

$$v^+ = V_2 \frac{R_2}{R_1 + R_2}$$


$$v^- = V_{out} + R_2 \frac{V_1 - V_{out}}{R_1 + R_2}$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

**Need a NEGATIVE power supply!** (Since  $V_{in}$  is inverted.)
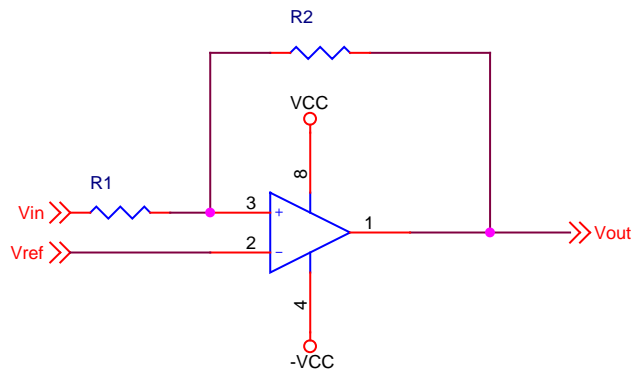
# Saturation

- **Positive feedback is unstable and usually leads to saturation of the output voltage**
  - **Positive Feedback is not very useful for linear tasks, but it can be useful for other jobs...**
  - **Create “digital” signals from analog sources**




$$v^+ = v^- = V_{ref}$$

$$i^+ = 0 \rightarrow v^+ = V_{out} + R_2 \frac{V_{in} - V_{out}}{R_1 + R_2}$$

$$V_{out} = \frac{R_1 + R_2}{R_1} V_{ref} - \frac{R_2}{R_1} V_{in}$$

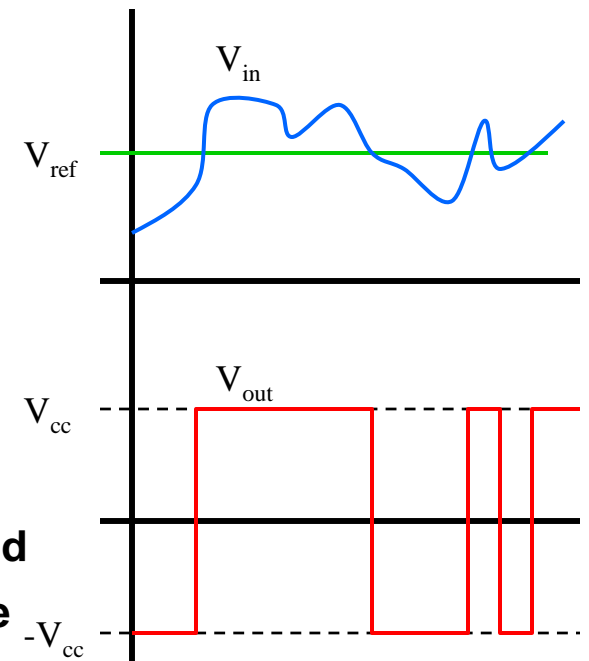
- **While the “ideal” math says that the system should be linear, in reality positive feedback saturates the output to the input voltages (+/- Vcc)**
  - **Can use  $R_2 = \infty$  (open, no feedback)**




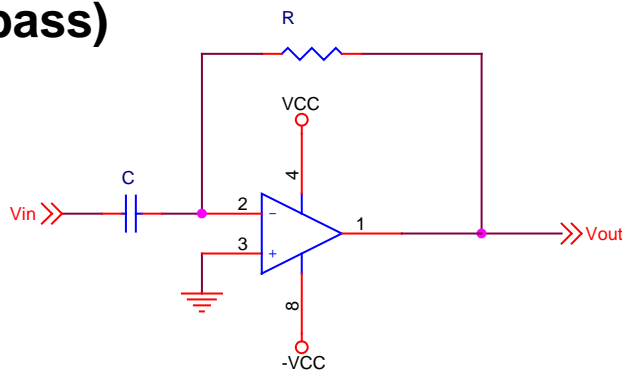
# Active Filters


- OpAmps allow active filtering of signals
  - The OpAmp provides power to follow the signals better
  - Feedback increases the performance of the filters
  - Enables to create both differentiators (high pass) and integrators (low pass)



$$v^+ = v^- = 0$$

$$i^- = 0 \rightarrow i_R = C \frac{dV_{in}}{dt}$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

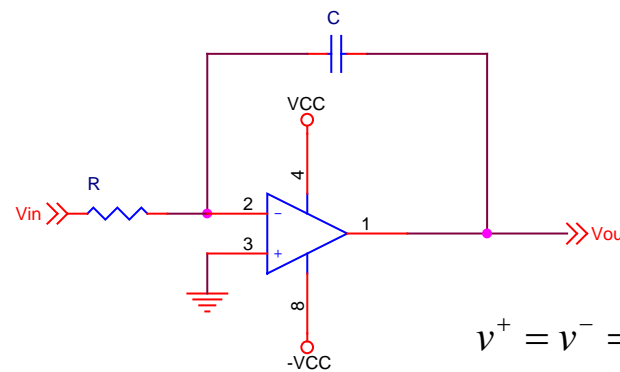

$$v^+ = v^- = 0$$

$$i^- = 0 \rightarrow i_R = \frac{V_{in}}{R}$$


$$V_C = \int \frac{V_{in}}{RC} dt$$

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$


# Real Operational Amplifiers

- Remember the non-ideal conditions

- **Ideal**

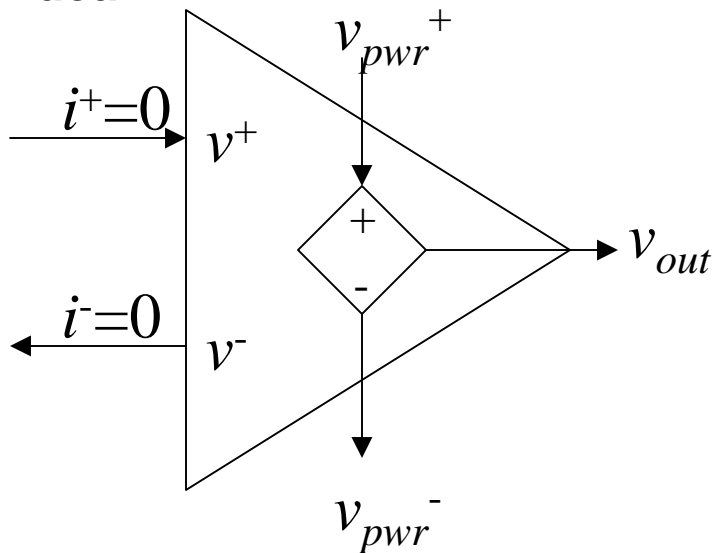

- **Real**

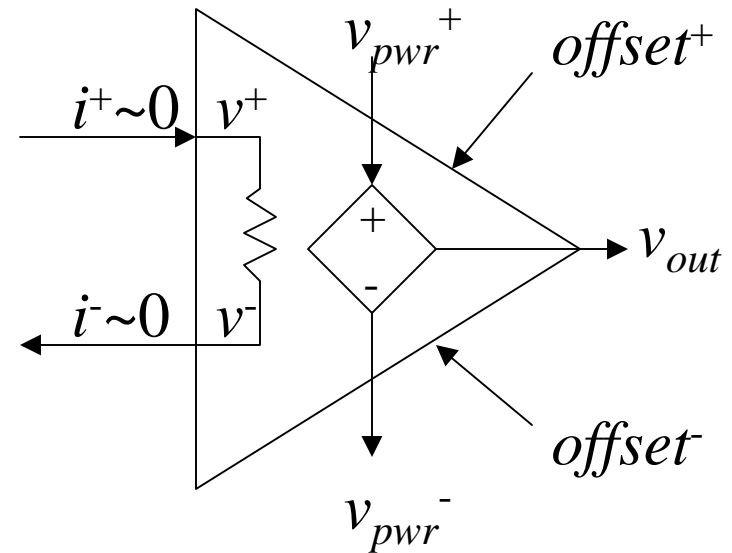

- **Non-linear**
- **Frequency dependent**
- **Offsets**
- **Saturation**
- **Hysteresis**
- **Temperature dependant**