


MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science

6.012
Microelectronic Devices and Circuits
Spring 2009

April 24, 2009 - Homework 7
Due May 1, 2009

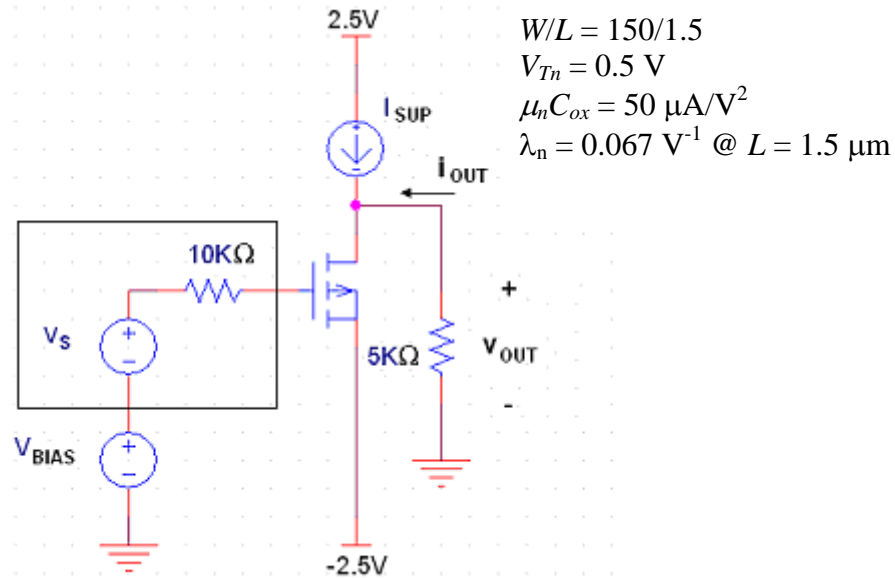Problem 1


You are given a CS amplifier and NMOS device parameters shown below. The current source supply provides $100\mu\text{A}$ and has an infinite output resistance, (i.e. $I_{\text{SUP}} = 100\mu\text{A}$ and $r_{oc} \rightarrow \infty$). The current source supply must have at least 0.5V across it in order to maintain the high output resistance.



- Calculate V_{BIAS} such that $V_{\text{OUT}} = 0\text{ V}$.
- Draw the two-port model and calculate the two-port parameters R_{in} , R_{out} , and A_v .
- Calculate the overall voltage gain v_{out}/v_s .
- Calculate the output voltage swing.

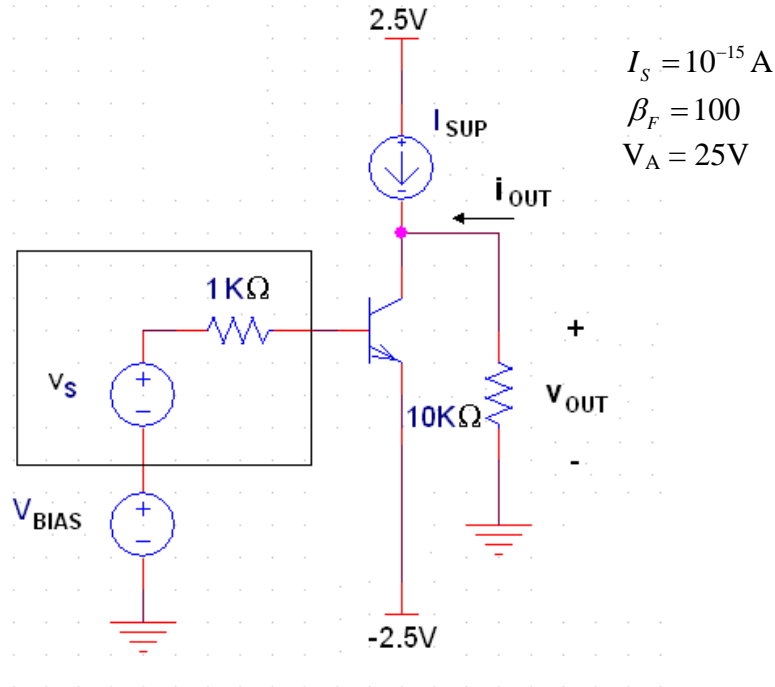Problem 2

You are given a CE amplifier and NPN device parameters shown below. The current source supply provides $250\mu\text{A}$ and has an output resistance equal to r_o of the NPN (i.e. $I_{SUP} = 250\mu\text{A}$ and $r_{oc} = r_o$). The current source supply must have at least 0.5V across it in order to maintain the high output resistance.



- Calculate V_{BIAS} such that $V_{OUT} = 0\text{V}$.
- Draw the two-port model and calculate the two-port parameters R_{in} , R_{out} , and A_v .
- Calculate the overall voltage gain v_{out}/v_s .
- Calculate the output voltage swing. Assume $V_{CEsat} = 0.2\text{V}$.

Problem 3

Howe and Sodini P8.30

Problem 4

Howe and Sodini P8.39, $V_{TON} = 0.7\text{V}$

MIT OpenCourseWare
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.