

Lecture 22

Frequency Response of Amplifiers (II)

VOLTAGE AMPLIFIERS


Outline

1. Full Analysis
2. Miller Approximation
3. Open Circuit Time Constant

Reading Assignment:


Howe and Sodini, Chapter 10, Sections 10.1-10.4

Common Emitter Amplifier

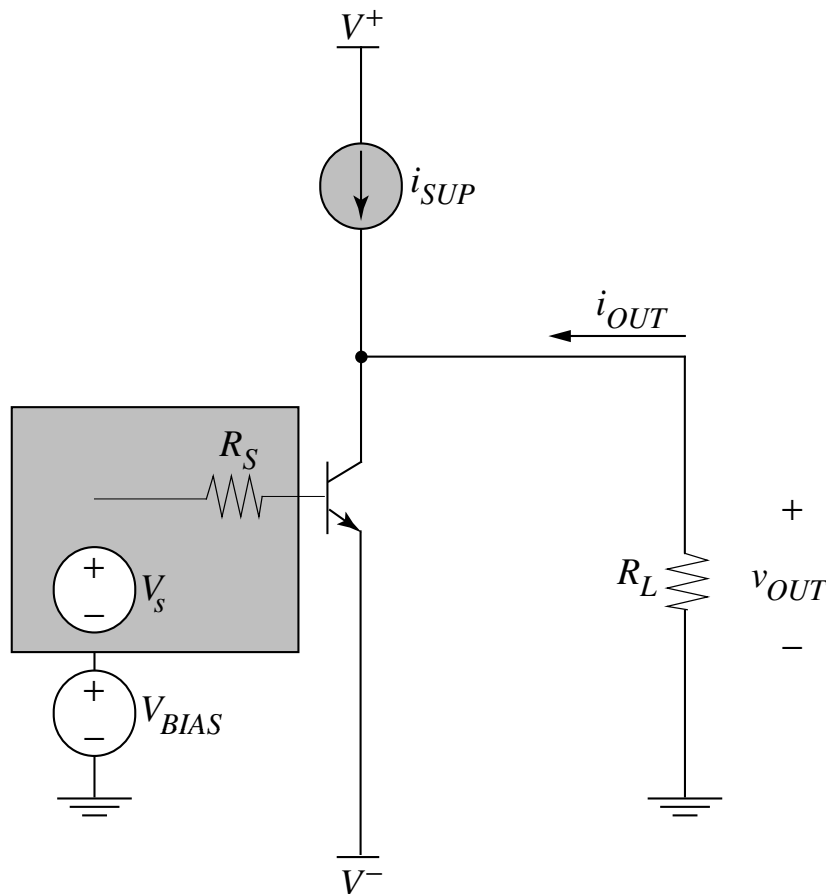


- Operating Point Analysis
 - $v_s=0, R_s=0, r_o \rightarrow \infty, r_{oc} \rightarrow \infty, R_L \rightarrow \infty$
 - Find V_{BIAS} such that $I_C=I_{SUP}$ with the BJT in the forward active region

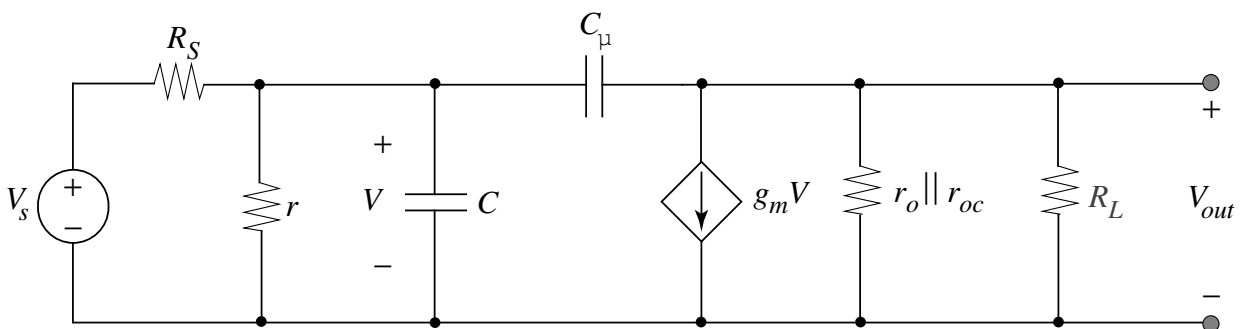Frequency Response Analysis of the Common Emitter Amplifier




- Frequency Response
 - Set $V_{BIAS} = 0$.
 - Substitute BJT small signal model (with capacitors) including R_S , R_L , r_o , r_{oc}
 - Perform impedance analysis

1. Full Analysis of CE Voltage Amplifier

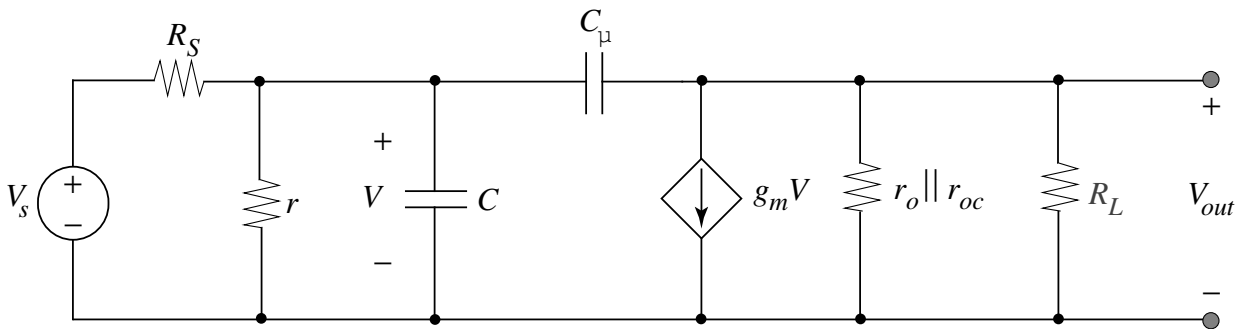

Replace voltage source and resistance with current source and resistance using Norton Equivalent

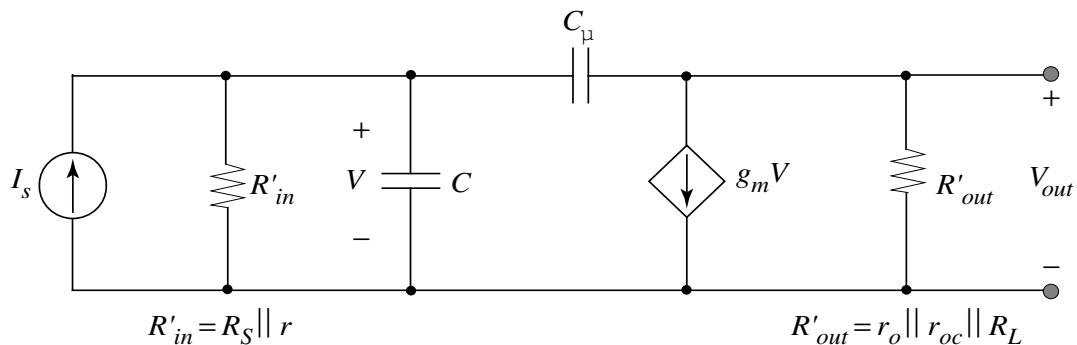

Node 1:

$$I_s = \frac{V_\pi}{R'_{in}} + j\omega C_\pi V_\pi + j\omega C_\mu (V_\pi - V_{out})$$

Node 2:

$$g_m V_\pi + \frac{V_{out}}{R'_{out}} = j\omega C_\mu (V_\pi - V_{out})$$

Full Frequency Response Analysis (contd.)

- Re-arrange **2** and obtain an expression for V_π
- Substituting it into **1** and with some manipulation, we can obtain an expression for V_{out} / I_s :

$$\frac{V_{out}}{I_s} = \frac{-R'_{in}R'_{out}(g_m - j\omega C_\mu)}{1 + j\omega(R'_{out}C_\mu + R'_{in}C_\mu + R'_{in}C_\pi + g_m R'_{out}R'_{in}C_\mu) - \omega^2 R'_{out}R'_{in}C_\mu C_\pi}$$

Changing input current source back to a voltage source:

$$\frac{V_{out}}{V_s} = \frac{-g_m R'_{out} \left(\frac{r_\pi}{R_s + r_\pi} \right) \left(1 - j\omega \frac{C_\mu}{g_m} \right)}{1 + j\omega(R'_{out}C_\mu + R'_{in}C_\mu(1 + g_m R'_{out}) + R'_{in}C_\pi) - \omega^2 R'_{out}R'_{in}C_\mu C_\pi}$$

where $R'_{in} = \mathbf{R}_S \parallel \mathbf{r}_\pi$ and $R'_{out} = \mathbf{r}_o \parallel \mathbf{r}_{oc} \parallel \mathbf{R}_L$


We can ignore zero at g_m/C_μ because it is higher than ω_T .

The gain can be expressed as:

$$\frac{V_{out}}{V_s} = \frac{A_{vo}}{(1 + j\omega\tau_1)(1 + j\omega\tau_2)} = \frac{A_{vo}}{1 - j\omega(\tau_1 + \tau_2) - \omega^2\tau_1\tau_2}$$

where A_{vo} is the gain at low frequency and τ_1 and τ_2 are the two time constants associated with the capacitors

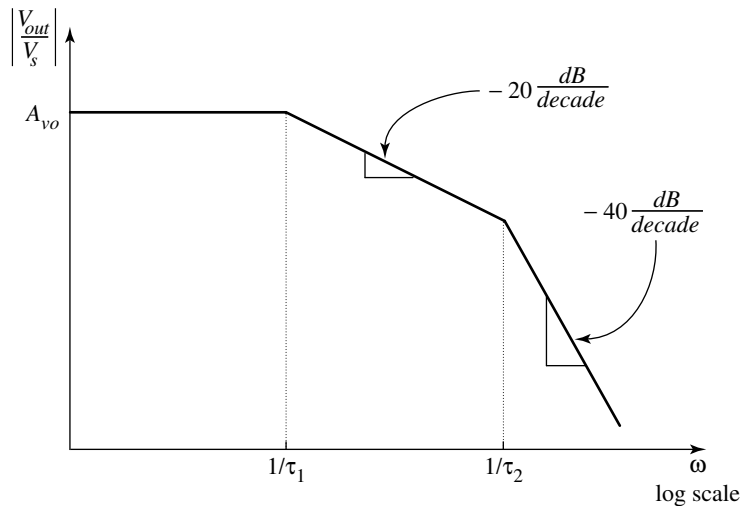Denominator of the System Transfer Function



$$\tau_1 + \tau_2 = R'_{out} C_{\mu} + R'_{in} C_{\mu} (1 + g_m R'_{out}) + R'_{in} C_{\pi}$$

$$\tau_1 \cdot \tau_2 = R'_{out} R'_{in} C_{\mu} C_{\pi}$$

We could solve for τ_1 and τ_2 but is algebraically complex.

- However, if we assume that $\tau_1 \gg \tau_2, \Rightarrow \tau_1 + \tau_2 \approx \tau_1$.
- This is a conservative estimate since the *true* τ_1 is actually smaller and hence the *true* bandwidth is actually larger than:


$$\tau_1 \approx R'_{in} \left[C_{\pi} + C_{\mu} (1 + g_m R'_{out}) \right] + R'_{out} C_{\mu}$$

Then:

$$\omega_{3dB} = \frac{1}{\tau_1} = \frac{1}{R'_{in} \left[C_{\pi} + C_{\mu} (1 + g_m R'_{out}) \right] + R'_{out} C_{\mu}}$$

2. The Miller Approximation

Effect of C_μ on the Input Impedance:

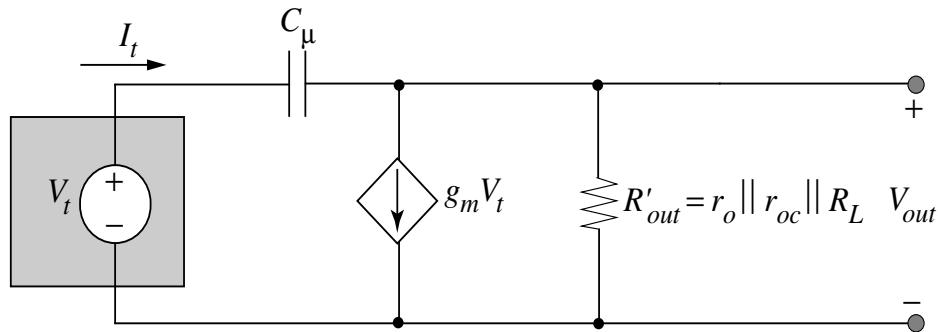

The input impedance Z_i is determined by applying a test voltage V_t to the input and measuring I_t :

$$V_{out} = -g_m V_t R'_{out} + I_t R'_{out}$$

The Miller Approximation assumes that current through C_μ is small compared to the transconductance generator

$$I_t \ll |g_m V_t|$$

$$V_{out} \approx -g_m V_t R'_{out}$$

We can relate V_t and V_{out} by

$$V_t - V_{out} = \frac{I_t}{j\omega C_\mu}$$


The Miller Approximation (contd.)

After some Algebra:

$$\frac{V_t}{I_t} = Z_{eff} = \frac{1}{j\omega C_\mu (1 + g_m R'_{out})} = \frac{1}{j\omega C_\mu (1 - A_{vC_\mu})}$$

The effect of C_μ at input is that C_μ is “Miller multiplied” by $(1 - A_{vC_\mu})$


Generalized “Miller Effect”

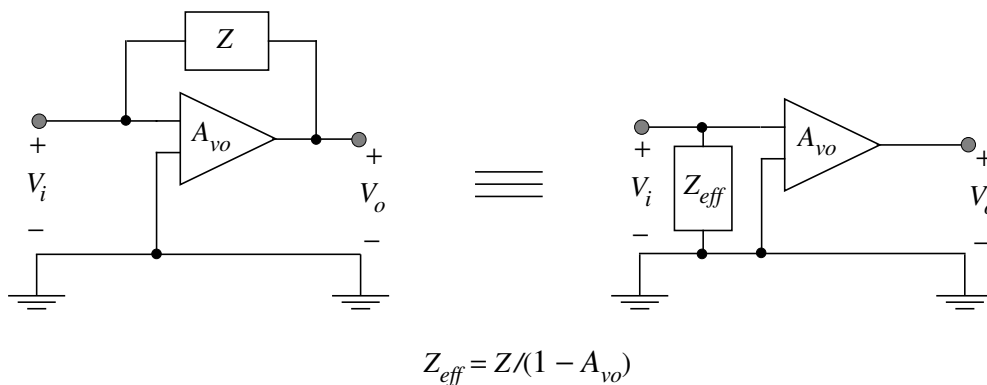

- An impedance connected across an amplifier with voltage gain A_{vo} can be replaced by an an impedance to ground ... divided by $(1 - A_{vo})$
- A_{vo} is large and negative for common-emitter and common-source amplifiers
- Capacitance at input is magnified.

$$Z_{eff} = \frac{Z}{(1 - A_{vo})}$$

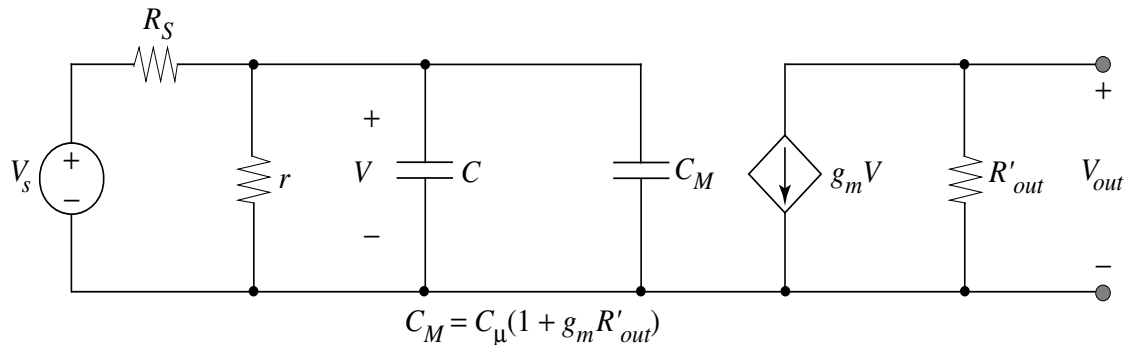Frequency Response of the CE Voltage Amplifier Using Miller Approximation



- The Miller capacitance is lumped together with C_{π} , which results in a single pole low pass filter at the input

$$\frac{V_{out}}{V_s} = -g_m \left(\frac{r_{\pi}}{r_{\pi} + R_S} \right) R'_{out} \left[\frac{1}{1 + j\omega(C_{\pi} + C_M)(R_S \parallel r_{\pi})} \right]$$

- At low frequency (DC) the small signal voltage gain is

$$\frac{V_{out}}{V_s} = -g_m \left(\frac{r_{\pi}}{r_{\pi} + R_S} \right) R'_{out}$$

- The frequency at which the magnitude of the voltage gain is reduced by $1/\sqrt{2}$ is

$$\omega_{3dB} = \frac{1}{(R_S \parallel r_{\pi})(C_{\pi} + C_M)} = \left[\frac{1}{(R_S \parallel r_{\pi})} \right] \left[\frac{1}{C_{\pi} + (1 + g_m R'_{out})C_{\mu}} \right]$$

3. Open Circuit Time Constant Analysis

Assumptions:

- No zeros
- One “dominant” pole ($1/\tau_1 \ll 1/\tau_2, 1/\tau_3 \dots 1/\tau_n$)
- N capacitors

$$\frac{V_{out}}{V_s} = \frac{A_{vo}}{(1 + j\omega\tau_1)(1 + j\omega\tau_2)(1 + j\omega\tau_n)}$$

The example shows a voltage gain; however, it could be I_{out}/V_s or V_{out}/I_s .

Multiplying out the denominator:

$$\frac{V_{out}}{V_s} = \frac{A_{vo}}{1 + b_1(j\omega) + b_2(j\omega)^2 + \dots + b_n(j\omega)^n}$$

$$\text{where } b_1 = \tau_1 + \tau_2 + \tau_3 + \dots + \tau_n$$

It can be shown that the coefficient b_1 can be found exactly [see Gray & Meyer, 3rd Edition, pp. 502-506]

$$b_1 = \left(\sum_{i=1}^N R_{Ti} C_i \right) = \left(\sum_i \tau_{C_{i0}} \right)$$

- $\tau_{C_{i0}}$ is the open-circuit time constant for capacitor C_i
- C_i is the i^{th} capacitor and R_{Ti} is the Thevenin resistance across the i^{th} capacitor terminals (with all capacitors open-circuited)

Open Circuit Time Constant Analysis

Estimating the Dominant Pole


The dominant pole of the system can be estimated by:

$$b_1 = \tau_1 + \tau_2 + \tau_3 + \dots + \tau_n$$
$$b_1 = \left(\sum_{i=1}^N R_{Ti} C_i \right) \approx \tau_1 = \frac{1}{\omega_1}$$


$R_{Ti} C_i$ is the **open-circuit time constant** for capacitor C_i

Power of the Technique:

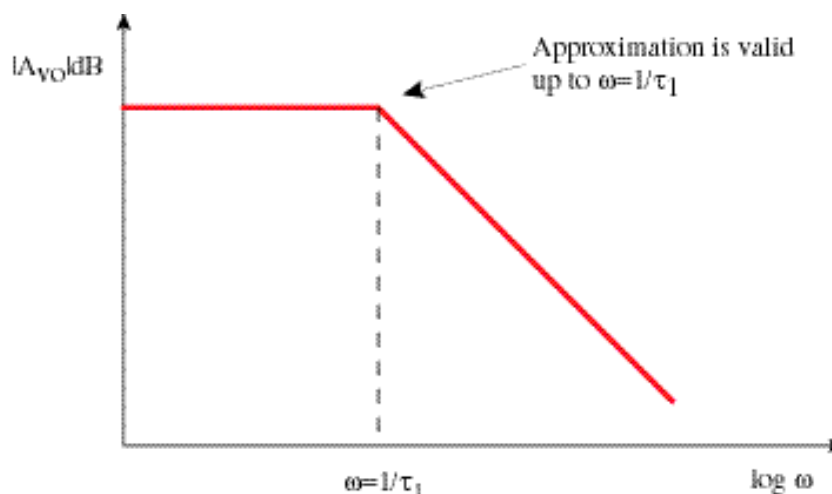- Estimates the contribution of each capacitor to the dominant pole frequency separately
- Enables the designer to understand what part of a complicated circuit is responsible for limiting the bandwidth of amplifier
- The approximate magnitude of the Bode Plot is



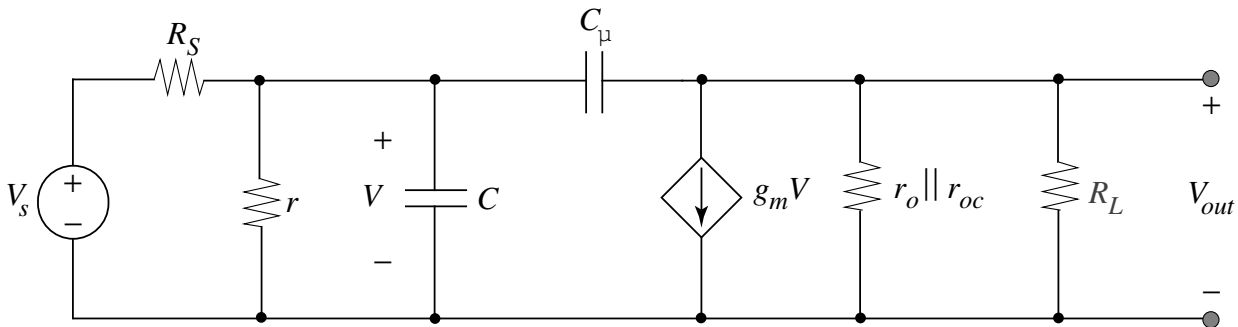Common Emitter Amplifier Analysis Using OCT



From the Full Analysis

$$\frac{V_{out}}{V_s} = \frac{-g_m R'_{out} \left(\frac{r_\pi}{R_S + r_\pi} \right) \left(1 - j\omega \frac{C_\mu}{g_m} \right)}{1 + j\omega (R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi) - \omega^2 R'_{out} R'_{in} C_\mu C_\pi}$$

where $R'_{in} = R_S \parallel r_\pi$ and $R'_{out} = r_o \parallel r_{oc} \parallel R_L$


$$b_1 = R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi$$

$$\omega_{3dB} \approx \frac{1}{b_1} = \frac{1}{R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi}$$

Common Emitter Amplifier Analysis Using OCT—Procedure

1. Eliminate all independent sources [e.g. $V_s \rightarrow 0$]
2. Open-circuit all capacitors
3. Find the Thevenin resistance by applying i_t and measuring v_t .

Time Constant for C_π

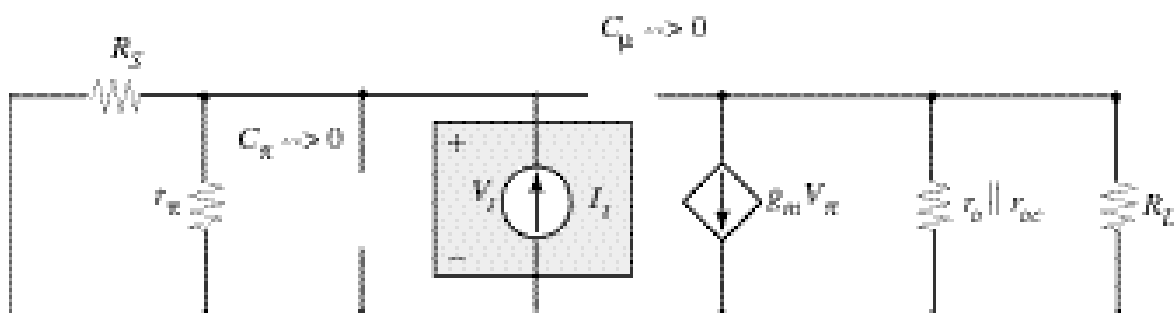


Result obtained by inspection

$$R_{T\pi} = R_S \parallel r_\pi$$


$$\tau_{C_\pi} = R_{T\pi} C_\pi$$

Common Emitter Amplifier Analysis Using OCT—Time Constant for C_μ

Using the same procedure

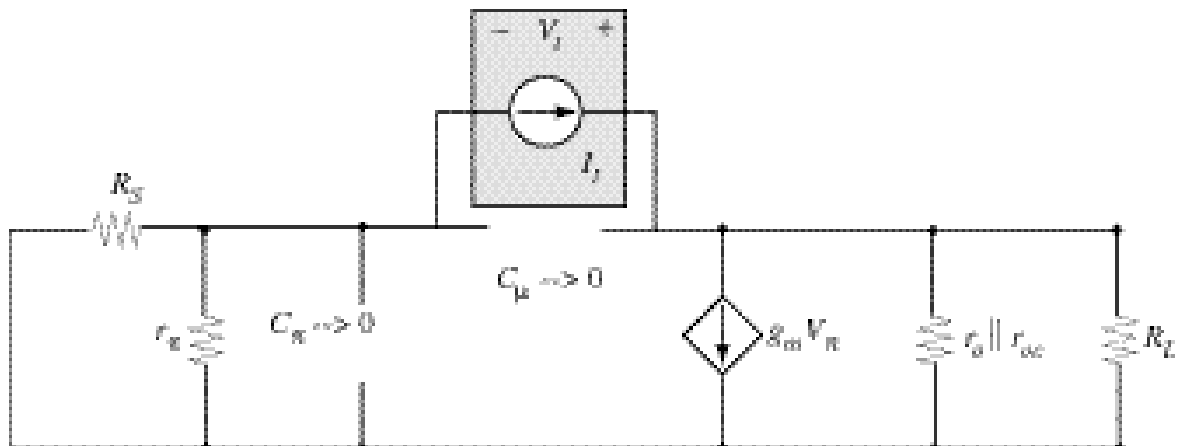

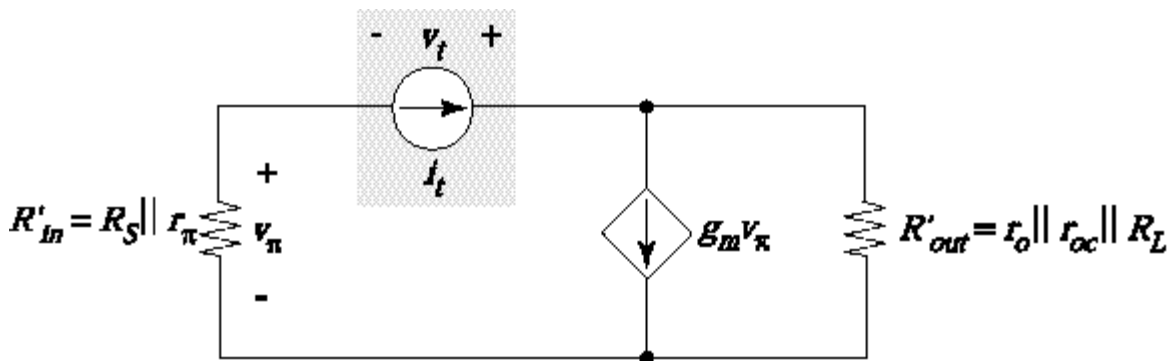Let $R'_{in} = R_S \parallel r_\pi$ and $R'_{out} = r_o \parallel r_{oc} \parallel R_L$



$$-i_t = \frac{v_\pi}{R'_{in}} \quad i_t = \frac{v_t + v_\pi}{R'_{out}} + g_m v_\pi \quad \text{Eliminate } v_\pi:$$

$$\frac{v_t}{i_t} = R_{T\mu} = R'_{out} + R'_{in}(1 + g_m R'_{out})$$

$$\tau_{C_{\mu o}} = R_{T\mu} C_\mu = [R'_{out} + R'_{in}(1 + g_m R'_{out})] C_\mu$$

Common Emitter Amplifier Analysis Using OCT—Dominant Pole

Summing individual time constants

$$b_1 = R_{T\pi} C_\pi + R_{T\mu} C_\mu$$

$$b_1 = R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi$$

Assume $\tau_1 \gg \tau_2$

$$b_1 = \tau_1 + \tau_2 \approx \tau_1$$

$$b_1 = R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi$$

$$\omega_{3dB} \approx \frac{1}{b_1} = \frac{1}{R'_{out} C_\mu + R'_{in} C_\mu (1 + g_m R'_{out}) + R'_{in} C_\pi}$$

This result is very similar to the Miller Effect calculation
Additional term $R'_{out} C_\mu$ taken into account

Compare the Three Methods of Analyzing the Frequency Response of CE Amplifier

Full Analysis—

$$\omega_{3dB} \approx \frac{1}{\tau_1} = \frac{1}{R'_{out}C_{\mu} + R'_{in}C_{\mu}(1 + g_m R'_{out}) + R'_{in}C_{\pi}}$$

Miller Approximation—

$$\omega_{3dB} = \left[\frac{1}{R'_{in}} \right] \left[\frac{1}{C_{\pi} + (1 + g_m R'_{out})C_{\mu}} \right]$$

Open Circuit Time Constant—

$$\omega_{3dB} \approx \frac{1}{b_1} = \frac{1}{R'_{out}C_{\mu} + R'_{in}C_{\mu}(1 + g_m R'_{out}) + R'_{in}C_{\pi}}$$

What did we learn today?

Summary of Key Concepts

- Full Analysis
 - Assumes that $\tau_1 + \tau_2 \approx \tau_1$

$$\omega_{3dB} \approx \frac{1}{\tau_1} = \frac{1}{R'_{out} C_{\mu} + R'_{in} C_{\mu} (1 + g_m R'_{out}) + R'_{in} C_{\pi}}$$

- Miller Approximation
 - Does not take into account R'_{out}

$$\omega_{3dB} = \left[\frac{1}{R'_{in}} \right] \left[\frac{1}{C_{\pi} + (1 + g_m R'_{out}) C_{\mu}} \right]$$

- Open Circuit Time Constant (OCT)
 - Assumes a dominant pole as full analysis

$$\omega_{3dB} \approx \frac{1}{b_1} = \frac{1}{R'_{out} C_{\mu} + R'_{in} C_{\mu} (1 + g_m R'_{out}) + R'_{in} C_{\pi}}$$

MIT OpenCourseWare
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.