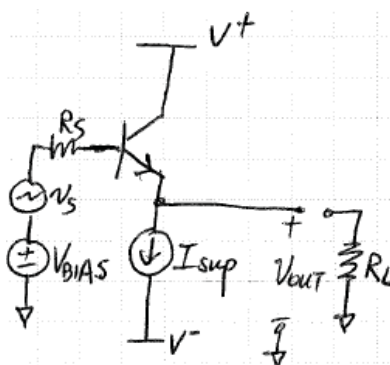


Recitation 23: Frequency Response of Common Collector & Common-Base Amplifier

Yesterday, we used OCT technique for the frequency response of Common-Drain and Common-Gate amplifiers. Today we will look at C-C, C-B frequency response.

Common-Collector Amplifier



One way to study the frequency response is to

- First find the small signal equivalent model for the circuit
- Do KCL, KVL nodal analysis, to find CO_{3dB}
- Or use OCT + Miller Approximation to find w_{3dB}


However, the small signal model of this circuit is quite complicated (as the C-D Amp. we talked about yesterday). What we can do is directly use the two-port model for the circuit, and add in the capacitances. So the methodology is as outlined below.

Methodology

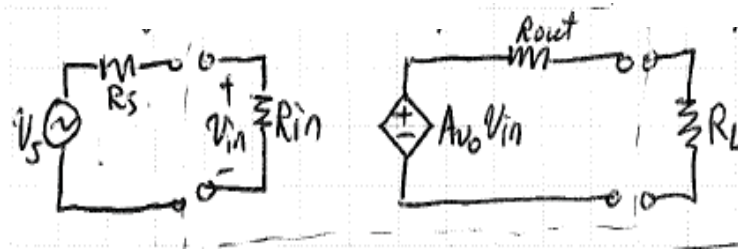1. Start with low frequency two port model, obtain Av, Ai, G_m at low frequency
2. Identify the nodes (S/D/G/B for MOS; B/E/C for BJT) and add in capacitance in active device
3. Use Miller Approximation in conjunction with OCT to estimate bandwidth (w_{3dB}).

Advantage: can directly use the " R_{in} ", " R_{out} " from two-port model, only need Av, Ai or G_m much easier.

So taking the C-C Amplifier as an example, the two port model is:




$$\begin{aligned}
 R_{in} &= \gamma_{\pi} + \beta_o(\gamma_o \parallel \gamma_{oc} \parallel R_L) \\
 R_{out} &= \frac{1}{g_m} + \frac{R_s}{\beta_o} \\
 A_{vo} &= 1 \\
 A_{v,LF} &= \frac{V_{out}}{V_s} = \frac{R_{in}}{R_s + R_{in}} \cdot (1) \cdot \frac{R_L}{R_L + R_{out}}
 \end{aligned}$$

Large g_m, β_o will give desired resistances for voltage buffer. High R_{in} , low R_{out}


$$= \frac{\gamma_{\pi} + \beta_o(\gamma_{oc} \parallel \gamma_o \parallel R_L)}{R_L + \gamma_{\pi} + \beta_o(\gamma_{oc} \parallel \gamma_o \parallel R_L)} (1) \frac{R_L}{R_L + \frac{1}{g_m} + \frac{R_s}{\beta_o}}$$

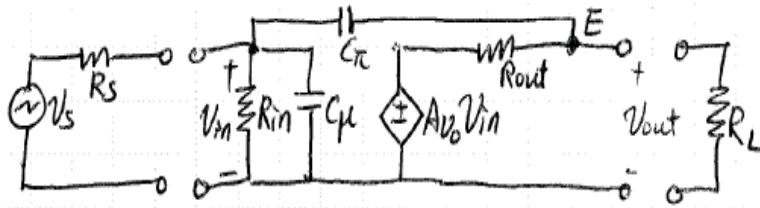Identify the B/E/C and add in capacitances



Note: the other end of C_{π} is to the right of R_{out} ! That is where "E" node is! C_{μ} is in the input/output feedback position.

Use Miller Approximation:

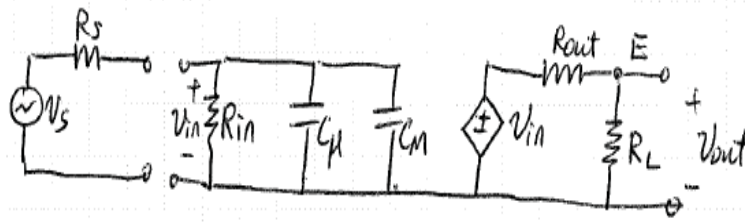

where $C_M = C_\pi(1 - A_{vC_\pi})$. A_{vC_π} is the voltage gain across C_π (not across overall amplifier).

What is the voltage gain across C_π ? $\frac{V_{out}}{V_{in}}$ instead of $\frac{V_{out}}{V_s}$

Or, it is $\frac{V_{out}}{V_s}$ when $R_s = 0$.

$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_s} \Big|_{R_s=0} = \frac{\gamma_\pi + \beta_o \overbrace{R_L}^{\text{typically } \gamma_o || \gamma_{oc} \gg R_L}}{R_s + \gamma_\pi + \beta_o R_L} (1) \frac{R_L}{R_L + \frac{1}{g_m} + \frac{R_s}{\beta_o}}$$

$$\therefore A_{vC_\pi} = \frac{R_L}{R_L + 1/g_m}$$


$$C_M = C_\pi(1 - A_{vC_\pi}) = C_\pi \left(\frac{1/g_m}{R_L + 1/g_m} \right) = C_\pi \left(\frac{1}{1 + g_m R_L} \right)$$

If $\frac{1}{g_m} \ll R_L$, then $A_{vC_\pi} \rightarrow 1 \implies C_M \rightarrow 0 \quad w_{3dB} = \frac{1}{(R_s || R_{in}) \cdot (C_\mu + C_M)}$

In contrast to C-S or C-E amplifier, the Miller effect reduces the capacitance in this case, which will give better frequency response: (or another way to look at it, effect of C_π is very small, since voltage gain across C_π is ≈ 1 . We do not need a lot of charges to go in/out the capacitor. And typically the movement of charges is the source to slow down the frequency response).


- Therefore like C-D, Miller effect reduces capacitor value, \implies expect good frequency response.
- Use of C-C: for multistage amplifiers, can enable high R_{in} , low R_{out} , won't degrade frequency response

Common-Base Amplifier

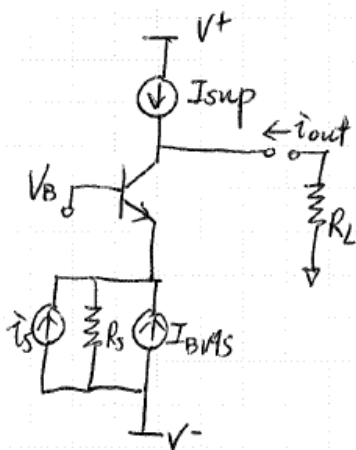

Current buffer:

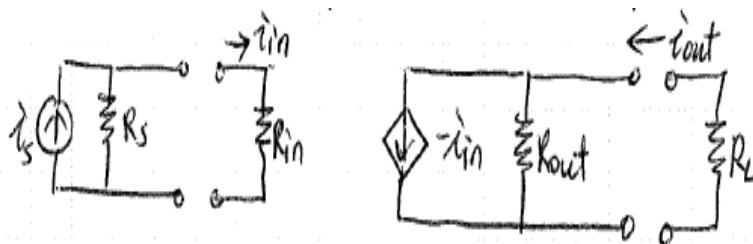1. Two port model (for current amplifier)




Low frequency current gain

$$\frac{i_{out}}{v_s} = \frac{R_s}{R_s + R_{in}} (-1) \frac{R_{out}}{R_{out} + R_L}$$

$$R_{in} = \frac{1}{g_m}$$

$$R_{out} = \gamma_{oc} \parallel [\gamma_o (1 + g_m (\gamma_{\pi} \parallel R_s))]$$

2. Label B/E/C, add in capacitances

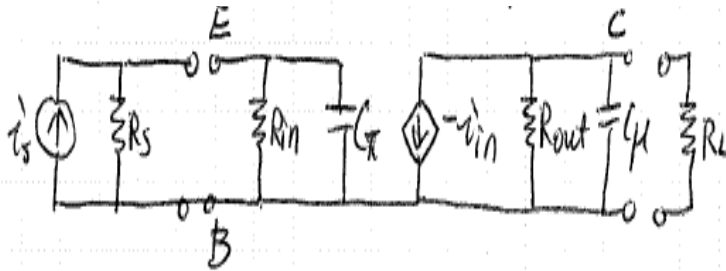

No capacitor in the feedback position \implies Do not need Miller Approximation. Use OCT

- C_π : $R_{TH_{C_\pi}} = R_s \parallel R_{in} = R_s \parallel \frac{1}{g_m}$
- C_μ : $R_{TH_{C_\mu}} = R_{out} \parallel R_L = R_L \parallel (\gamma_{oc} \parallel (\gamma_o + g_m \gamma_o (\gamma_\pi \parallel R_s)))$

Let us try to make some simplifications (if conditions are met) for a on w_{3dB} :

If R_s not so small, since $\frac{1}{g_m}$ is small ($\sim 100\Omega$),

$$R_s \parallel \frac{1}{g_m} \simeq \frac{1}{g_m} \implies T_{C_\pi} = \frac{C_\pi}{g_m}$$

$$\text{And if } R_s \gg \gamma_\pi (\sim 10 \text{ k}\Omega)$$

$$R_{out} = \gamma_{oc} \parallel (\gamma_o + g_m \gamma_o (\gamma_\pi \parallel R_s))$$

$$g_m \gamma_o (\gamma_\pi \parallel R_s) = g_m \gamma_\pi \gamma_o = \beta_o \gamma_o$$

$$R_{out} \longrightarrow \gamma_{oc} \parallel \beta_o \gamma_o \text{ can be quite large}$$

$$\implies R_{TH_{C_\mu}} \simeq R_L \parallel (\gamma_{oc} \parallel \beta_o \gamma_o) \simeq R_L$$

$$w_{3dB} \simeq \frac{1}{\frac{C_\pi}{g_m} + C_\mu R_L} \text{ can be approaching } w_T = \left(\frac{g_m}{C_\pi + C_\mu R_L} \right) - \text{a good current buffer}$$

MIT OpenCourseWare
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.