


MASSACHUSETTS INSTITUTE OF TECHNOLOGY
 6.071 Introduction to Electronics, Signals and Measurement
 Spring 2006

Laboratory 20: Introduction to the Op-Amp


In this lab we will explore the fundamental non-inverting (op-amp) amplifier circuit.

To construct the circuit we will use the LF356 op amp. The 356 is a good, cheap, easy to work with op amp well suited to most basic circuits. More expensive op amps tend to sacrifice op-amp ideality (finite input current, stability, power supply reject, etc.) for specific purposes (high speed, low noise etc.) and can be much more difficult to work with. The data sheet for the 356 is available in the class web site.

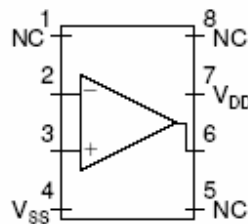The pinout of the 356 is the same as that of another widely used op amp, the 741, and is shown below.



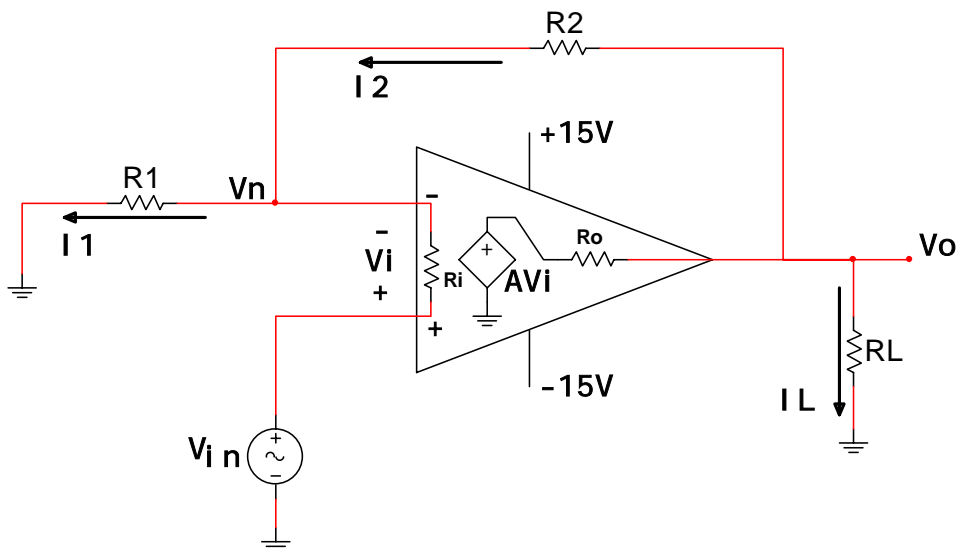Use this op-amp to construct the circuit shown below. Select R_1 and R_2 to achieve a gain of 3.



Make the following connections to your data acquisition system

ACH0+, Supply+ : V_{in}
ACH1+ : V_o
ACH2+ : V_n
 V_{DD} : +15 Volts
 V_{SS} : -15 Volts
ACH0-, ACH1-, ACH2- : Ground

Down load the LabView instrument called **Op-Amp1.vi** from the Labs section. Run the instrument and answer the following questions

1. For $V_{in}=2$ Volt measure and record the following

$V_n=$
 $V_o=$
 $I_1=$
 $I_2=$
 $I_L=$

Compare I_1 and I_2 . How close are they? What about V_n and V_i ?

2. Does $I_1+I_2+I_L$ satisfy KCL? If not what other currents should be considered?

3. A is the open loop gain of the op-amp. R_i and R_o are the input and output resistance of the op-amp device (NOT THE CIRCUIT THAT YOU HAVE CONSTRUCTED)

What value of A results in a 5% difference between the measured and the simulated output voltage V_o ?

4. For $V_{in} > 5$ Volts what is the output?

5. For $V_{in} = -2$ Volts What is V_o ?

6. Arrange your circuit to be a follower by making $R_2 = 0$ and $R_1 = \text{infinity}$. Observe the circuit operation. Justify your observation.