

MASSACHUSETTS INSTITUTE OF TECHNOLOGY

Department of Electrical Engineering and Computer Staff

6.301 Solid State Circuits

Fall Term 2010

Problem Set 7

Issued : Nov. 6, 2010

Due : Friday, Nov. 12, 2010

**Suggested Reading:** Read as many of the following as you can. All of the recommended references are on reserve at Barker Library.


1. Lundberg sections 30 and 33–36.
2. Grebene sections 7.3 and (skim) 9.
3. Gray and Meyer sections 6.2–6.4 and 10.3.

**Problem 1:** A basic operational amplifier circuit with an NPN input stage is shown on the next page. Calculate the following amplifier parameters.


- (a) Input Bias Current.
- (b) DC Small-Signal Differential Gain.
- (c) Common-Mode Rejection Ratio.
- (d) Compensation capacitor size to achieve 45 degrees of phase margin for unity-gain feedback. Hint: phase margin can be found from a Bode plot as the difference between the phase and -180 degrees when the magnitude is unity. That is, for 45 degrees of phase margin, the phase of the system must be -135 degrees when the magnitude is one.

Assume the following transistor parameters:

	NPN	PNP
$\beta$	200	40
$V_A$	50 V	20 V
$\tau_F$	2.5 ns	25 ns
$r_b, r_c$	0	0
$c_\mu, c_{je}, c_{cs}$	0	0

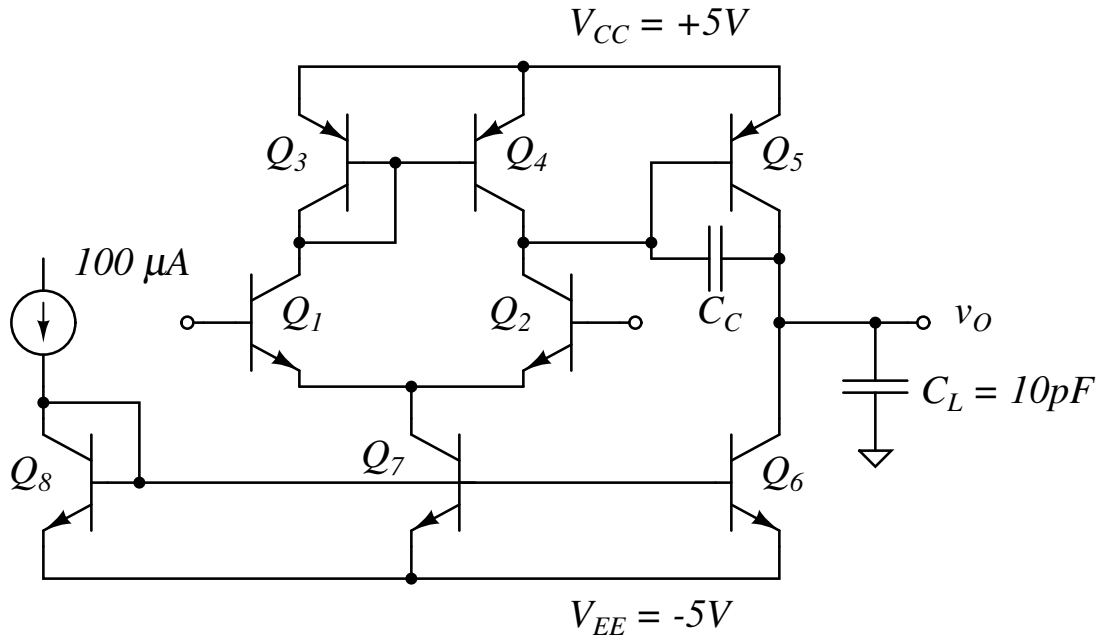





**Problem 2:** Repeat Problem 1 for the following PNP input operational amplifier. Create a summary table on the first page of your problem set comparing the values found in each layout.



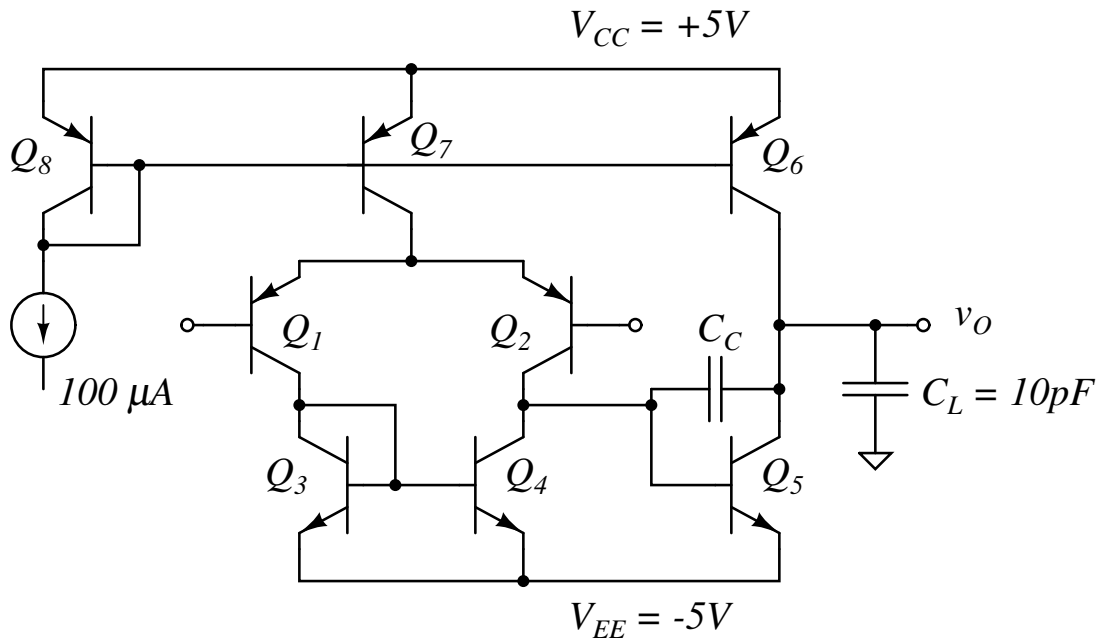


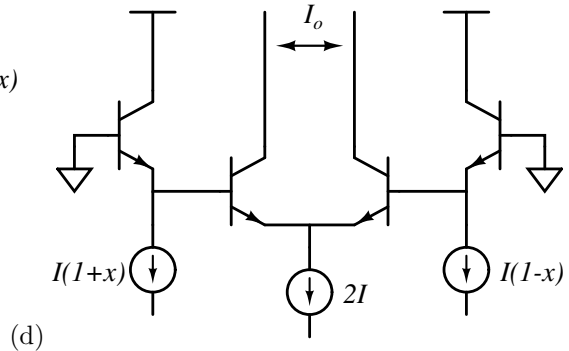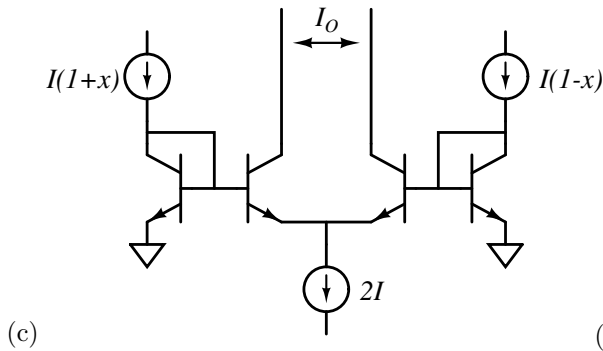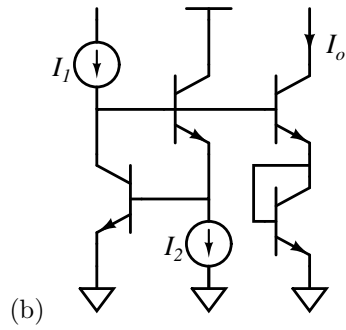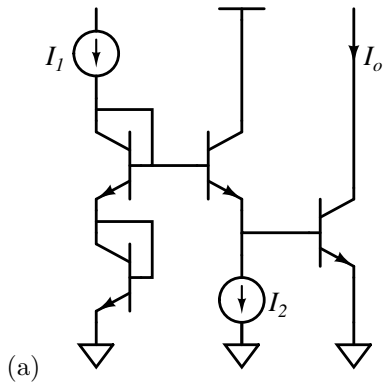**Problem 3:** For each of the following circuits use the “Gilbert Principle” to determine  $I_o$  as a function of the other circuit variables. All of these circuits simplify to simple expressions.

A differential output is denoted by an  $I_o$  superimposed on an arrow, and double emitter arrows with  $2A_E$  indicate that transistor has double the emitter area of the other transistors, thus its  $I_S$  is twice as large.


Finally, use the method of open circuit time constants to estimate the  $-3\text{dB}$  frequency for the circuit in part (a) only.



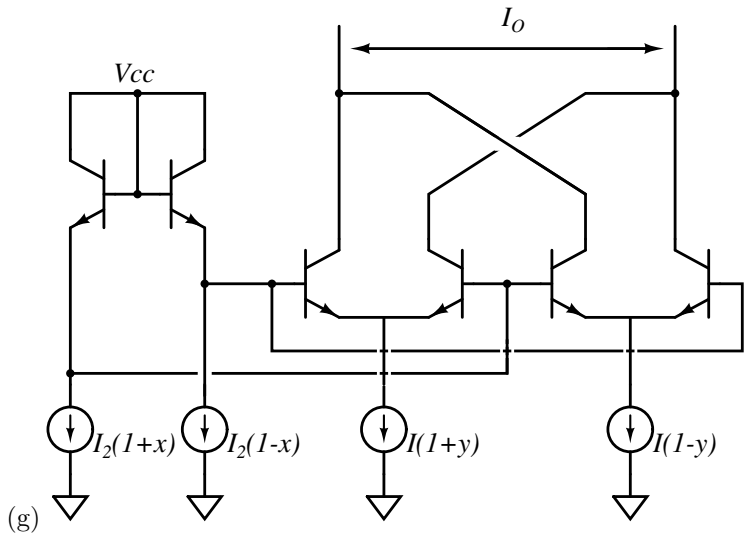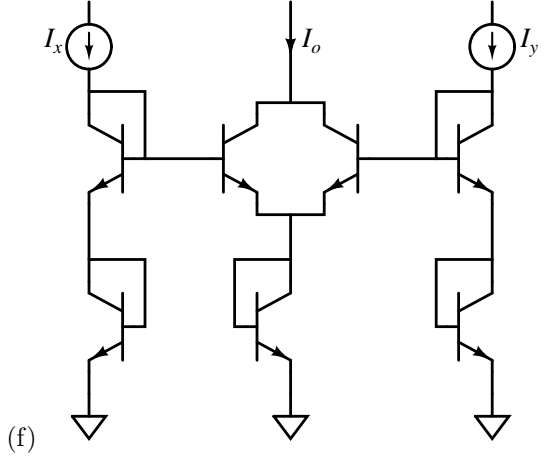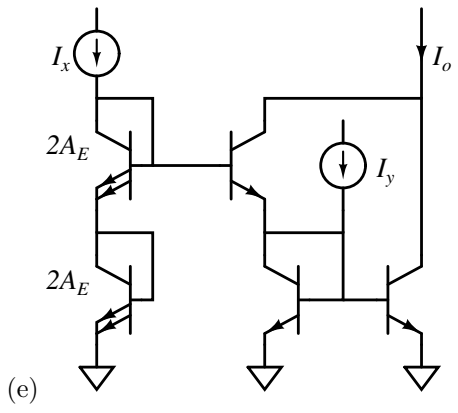

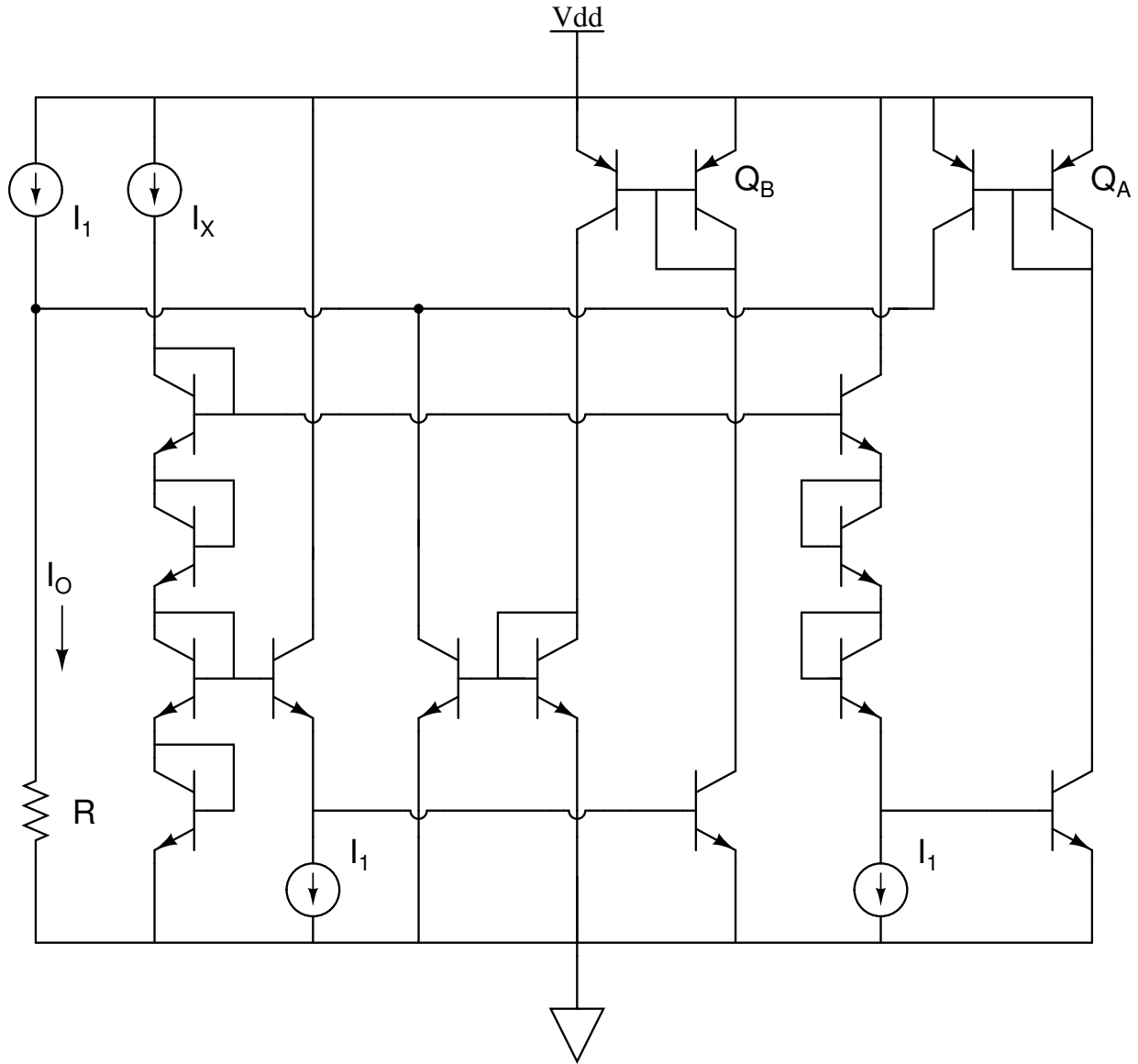**Problem 4:** Find  $I_o = f(I_x)$ , assuming well-matched transistors, negligible base currents and  $I_1 = 1\text{A}$ . Also, assume  $Q_A$  and  $Q_B$  have respective emitter areas  $24A_E$  and  $2A_E$  while all other transistors have emitter area  $A_E$ .

What famous function does  $I_o$  approximate for small  $I_x$ ?



MIT OpenCourseWare  
<http://ocw.mit.edu>

6.301 Solid-State Circuits  
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.