

## 6.301 Solid-State Circuits

Recitation 18: “Pythagorators,” and other circuits  
Prof. Joel L. Dawson


---

Way back at the beginning of the term, in Recitation 2, we talked about what it means to do engineering design. Quoting from those notes:

“In engineering design, we make use of nature’s laws to build useful machines.”

The Gilbert Principle is a classic example of how we use the exponential  $I_C$  vs.  $V_{BE}$  relationship to build analog computation elements. Before examining this in more detail, let’s use the class exercise to look at another intriguing case.

CLASS EXERCISE: Consider the following

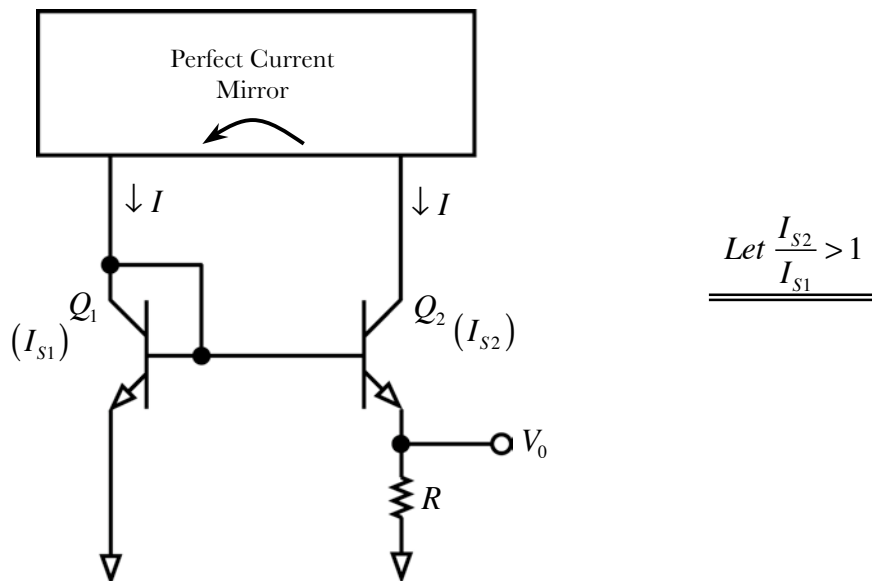

Using KVL, write  $V_0$  as a function of  $I$ ,  $I_{S1}$ , and  $I_{S2}$ . Can you think of any useful function served by  $V_0$ ?

(Workspace)

## 6.301 Solid-State Circuits

Recitation 18: "Pythagorators," and other circuits  
Prof. Joel L. Dawson

---

How about that?! Note that while the temperature dependence of  $V_{BE}$  is complicated, the temperature dependence of a  $\Delta V_{BE}$  is simple:

$$\Delta V_{BE} = \frac{kT}{q} \ln\left(\frac{I_{C1}}{I_S}\right) - \frac{kT}{q} \ln\left(\frac{I_{C2}}{I_S}\right) = \frac{kT}{q} \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$

If  $\frac{I_{C1}}{I_{C2}}$  is independent of temperature, we say that  $\Delta V_{BE}$  is "PTAT," or

Proportional to Absolute Temperature.


So...we took advantage of our detailed knowledge of bipolar transistors to build a thermometer. The Gilbert Principle takes advantage of our knowledge in a different way, and for a different end.

Final Note: Do not use circuits like the class exercise without some sort of start-up circuitry. Note that  $I=0$  is a valid state.

---

As we saw in lecture yesterday, the Gilbert Principle is a kind of mathematical shorthand for KVL. Let's review.

Current square-root circuit:

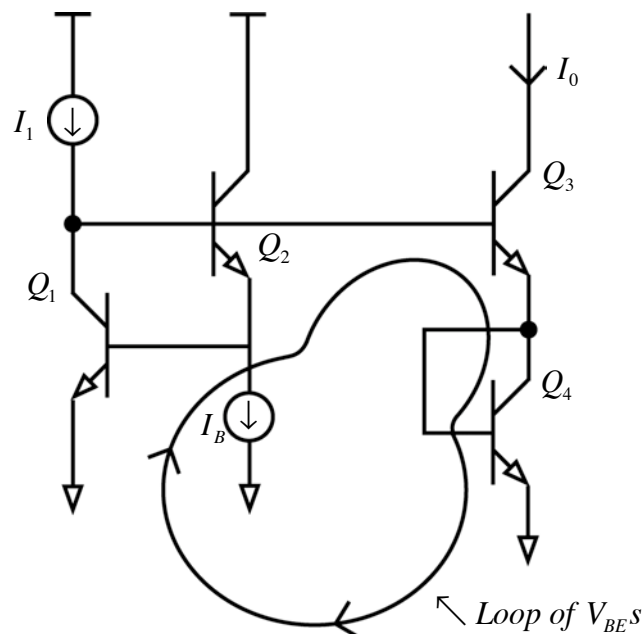

## 6.301 Solid-State Circuits

Recitation 18: "Pythagorators," and other circuits

Prof. Joel L. Dawson

---

Write out KVL:

$$V_{BE1} + V_{BE2} - V_{BE3} - V_{BE4} = 0$$

$$V_T \ln\left(\frac{I_1}{I_S}\right) + V_T \ln\left(\frac{I_B}{I_S}\right) - V_T \ln\left(\frac{I_0}{I_S}\right) - V_T \ln\left(\frac{I_0}{I_S}\right) = 0$$

$$\cancel{V_T} \ln\left(\frac{I_1 I_B}{I_S^2}\right) = \cancel{V_T} \ln\left(\frac{I_0^2}{I_S^2}\right)$$


$$I_0 = \sqrt{I_B I_1} = k \sqrt{I_1}$$

Pretty neat. From this example, simple though it is, we can draw a couple of very general conclusions.

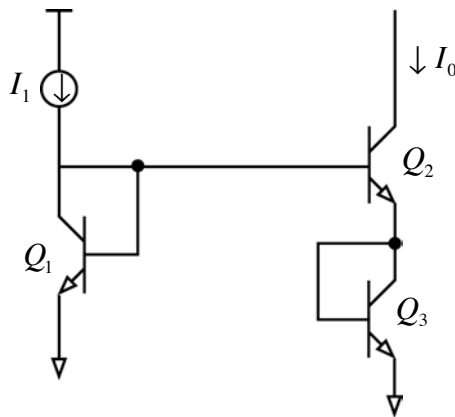- (1) Translinear circuits are fast.
- (2) Translinear circuits always involve an even number of  $V_{BE}$ 's.

To understand (1), look at all of the  $C_{\mu}$ 's. None of them get Miller multiplied.  $C_{\mu1}$  Even gets bootstrapped, while  $C_{\mu4}$  gets shorted out altogether.

To understand (2), consider a tempting but extremely wrong way to implement the square root function.



Translinear principle:

$$I_1 = I_0^2$$

$$I_0 = \sqrt{I_1}$$

NO!!

(The units don't even work.)

## 6.301 Solid-State Circuits

Recitation 18: “Pythagorators,” and other circuits

Prof. Joel L. Dawson

---

KVL:

$$V_T \ln\left(\frac{I_1}{I_S}\right) = 2V_T \ln\left(\frac{I_0}{I_S}\right)$$

$$\ln\left(\frac{I_1}{I_S}\right) = \ln\left(\frac{I_0^2}{I_S^2}\right)$$

$$I_0 = \sqrt{I_S} \sqrt{I_1}$$

Vitally important that all of the  $I_S$  s cancel out. This is only possible if the number of CW  $V_{BE}$  s equals the number of CCW  $V_{BE}$  s.

To finish off the basics, we recall that we sometimes have the freedom to change emitter areas. If we write

$$I_S = A_E J_S$$

We have

$$\sum_{CW} V_{BE_m} = \sum_{CCW} V_{BE_n}$$

$$\prod_{CW} \frac{I_{C_m}}{I_{S_m}} = \prod_{CCW} \frac{I_{C_n}}{I_{S_n}}$$

$$\prod_{CW} \frac{I_{C_m}}{A_{E_m} J_S} = \prod_{CCW} \frac{I_{C_n}}{A_{E_n} J_S}$$

$$\prod_{CW} \frac{I_{C_m}}{A_{E_m}} = \prod_{CCW} \frac{I_{C_n}}{A_{E_n}}$$

This is the most general translinear principle.


## 6.301 Solid-State Circuits

Recitation 18: "Pythagorators," and other circuits

Prof. Joel L. Dawson

---

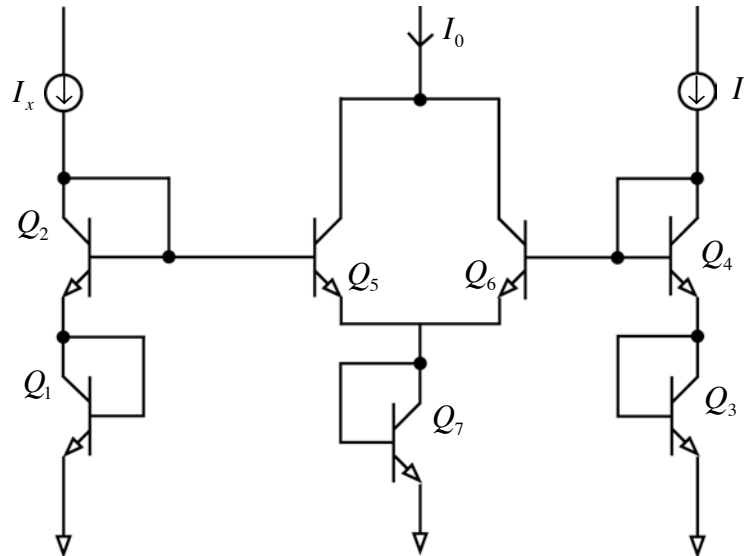Now, at last, a Pythagorator. One such cell was shown to you in lecture yesterday. Here is a seven-transistor version.



How to analyze? Start with

$$I_0 = I_5 + I_6$$

And

$$I_7 = I_0$$

The left Gilbert loop gives:

$$I_1 I_2 = I_5 I_7 = I_5 I_0$$

$$I_x^2 = I_5 I_0 \Rightarrow I_5 = \frac{I_x^2}{I_0}$$

Right Gilbert loop gives:

$$I_6 = \frac{I_y^2}{I_0}$$

So for the output:

$$I_0 = I_5 + I_6 = \frac{I_x^2}{I_0} + \frac{I_y^2}{I_0}$$

$$I_0^2 = I_x^2 + I_y^2$$

$$I_0 = \sqrt{I_x^2 + I_y^2}$$

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.301 Solid-State Circuits  
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.