

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Electrical Engineering and Computer Science

Problem Set No. 8  
Fall Term 2006


6.630 Electromagnetics

Issued: Week 9  
Due: Week 10

**Reading assignment:** Section 2.4, 2.6; J. A. Kong, “*Electromagnetic Wave Theory*”.

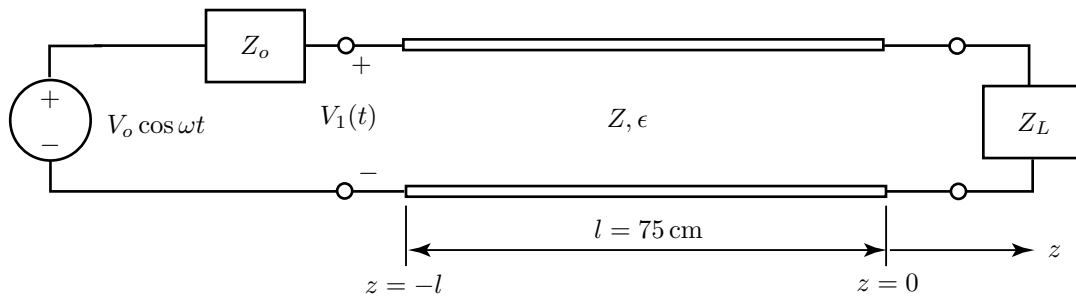**Problem P8.1**

A TEM transmission line is driven by a voltage source  $V_o \cos \omega t$  at 100 MHz. The characteristic impedance of the transmission line is  $Z_o = 100 \Omega$  for  $\epsilon = \epsilon_o$ . The transmission line length is  $l = 75 \text{ cm}$



(a) Let  $\epsilon = \epsilon_o$ , show that  $l = \lambda/4$ . If the voltage at  $z = -l$  is

$$V_1(t) = \frac{1}{\sqrt{2}} V_o \cos \left( \omega t - \frac{\pi}{4} \right),$$

what is the load impedance  $Z_L$ ?

(b) Let  $\epsilon = 4\epsilon_o$ , find the wavelength  $\lambda$ . What is the input impedance  $Z_{in}$  at  $z = -l$ ? What is the voltage  $V_1(t)$  at  $z = -l$ ?

**Problem P8.2**

Convert the following time domain expressions into their complex equivalents in the frequency domain, where we have defined

$$A = \text{Re} [\underline{A} e^{j\omega t}]$$

Example :  $A = \sin \omega t \quad \underline{A} = -j$

(a) Find  $\underline{A}$ .

(i)  $A = 3 \sin \left( \omega t - \frac{\pi}{4} \right)$

(ii)  $A = \hat{x} \sin \omega t - \hat{y} 2 \cos \omega t$

(iii)  $A = \cos \phi \cos \omega t$

(b) Find  $A$ .


(i)  $\underline{A} = j e^{j\pi/4}$

(ii)  $\underline{A} = \hat{x} + \hat{y} 3j$

(iii)  $\underline{A} = A_0 e^{j\phi} + j$

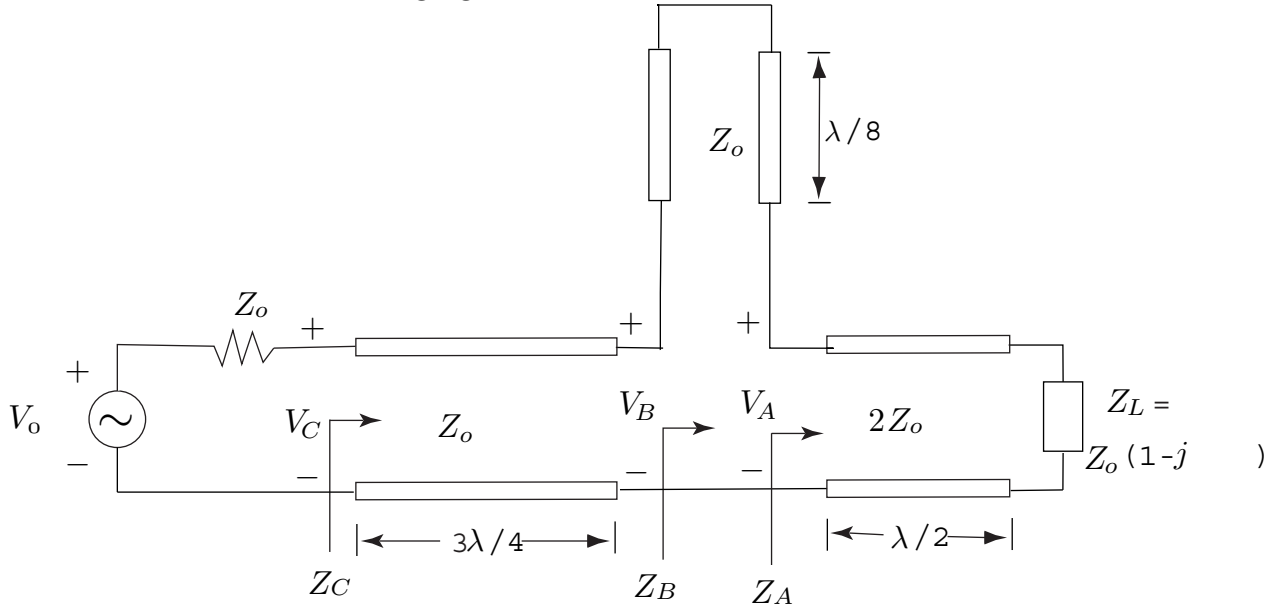**Problem P8.3**

Consider the TEM transmission line system connected to a time-harmonic voltage source as shown in the following figure.



- Find the impedance  $Z_A$  in terms of  $Z_o$ .
- Find the impedance  $Z_B$  in terms of  $Z_o$ .
- Find the impedance  $Z_C$  in terms of  $Z_o$ .
- Show that the time average power dissipated in  $Z_C$  is  $|V_o|^2/8Z_o$ . Assume  $Z_o$  is real.
- Find the voltage  $V_L$  across the load  $Z_L$  in terms of  $V_o$  and use  $V_L$  to calculate the time average power dissipated in the load  $Z_L$  in terms of  $V_o$  and  $Z_o$ . Assume  $Z_o$  is real.