

$$V_o = 10 \text{ Volt}$$

$$R = 10 \ \Omega$$

$$L = 5 \times 10^{-2} \text{ H}$$

$$C = 3 \times 10^{-7} \text{ F}$$

$$\omega_o = \frac{1}{\sqrt{LC}} \approx 8.2 \times 10^3 \text{ rad/s}$$

$$f_o \approx 1.3 \text{ kHz}$$

$$Z = \sqrt{R^2 + X^2}$$

ω rad/s	ωL Ω	-	$\frac{1}{\omega c}$ Ω	=	X Ω	Z Ω	I_{max} A
$0.9\omega_o$	367	-	453		-86	87	0.11
ω_o	408	-	408		0	10	1
$1.1\omega_o$	449	-	370		+78	79	0.12