

# Class 10: Outline

Hour 1:

DC Circuits

Hour 2:

Kirchhoff's Loop Rules

# Last Time: Capacitors & Dielectrics

# Capacitors & Dielectrics

## Capacitance

$$C = \frac{Q}{|\Delta V|}$$

To calculate:

- 1) Put on arbitrary  $\pm Q$
- 2) Calculate  $E$
- 3) Calculate  $\Delta V$

## Energy



$$U = \frac{Q^2}{2C} = \frac{1}{2} Q |\Delta V| = \frac{1}{2} C |\Delta V|^2 = \iiint u_E d^3 r = \iiint \frac{\epsilon_0 E^2}{2} d^3 r$$

## Dielectrics

$$\oiint_S \kappa \vec{E} \cdot d\vec{A} = \frac{q_{inside}^{free}}{\epsilon_0} \Rightarrow C_{\text{Filled with Dielectric}} = \kappa C_0$$

# **This Time: DC Circuits**

# Examples of Circuits

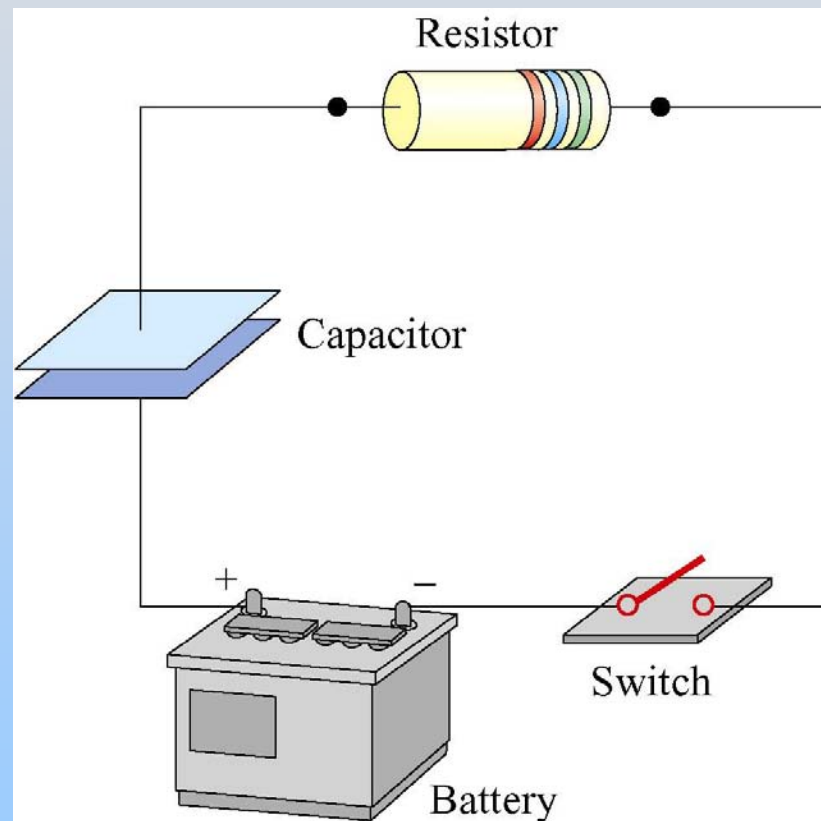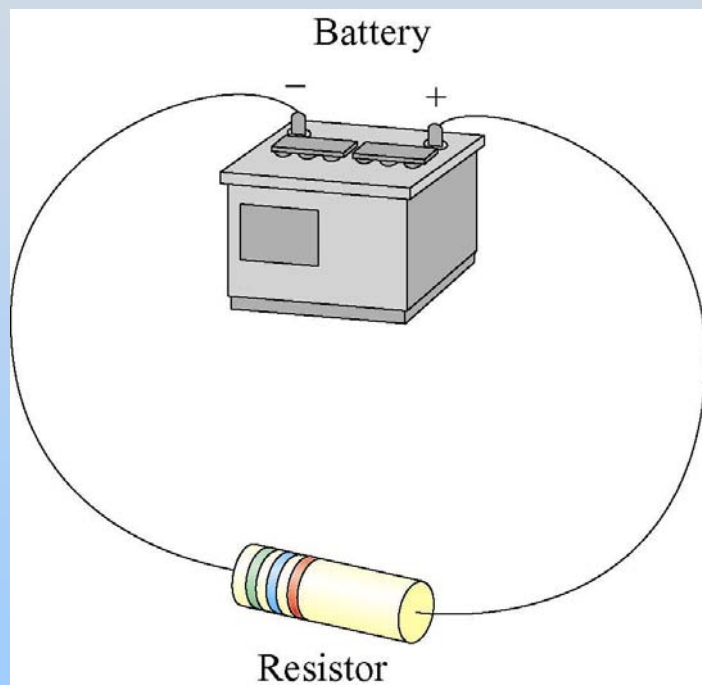


# Current: Flow Of Charge

Average current  $I_{av}$ : Charge  $\Delta Q$  flowing across area  $A$  in time  $\Delta t$

$$I_{av} = \frac{\Delta Q}{\Delta t}$$

Instantaneous current: differential limit of  $I_{av}$


$$I = \frac{dQ}{dt}$$

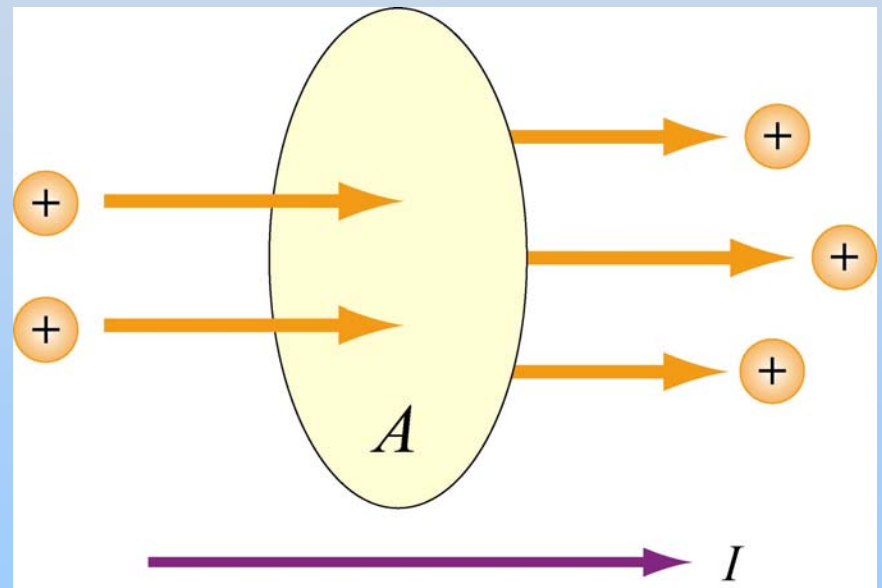


**Units of Current: Coulombs/second = Ampere**
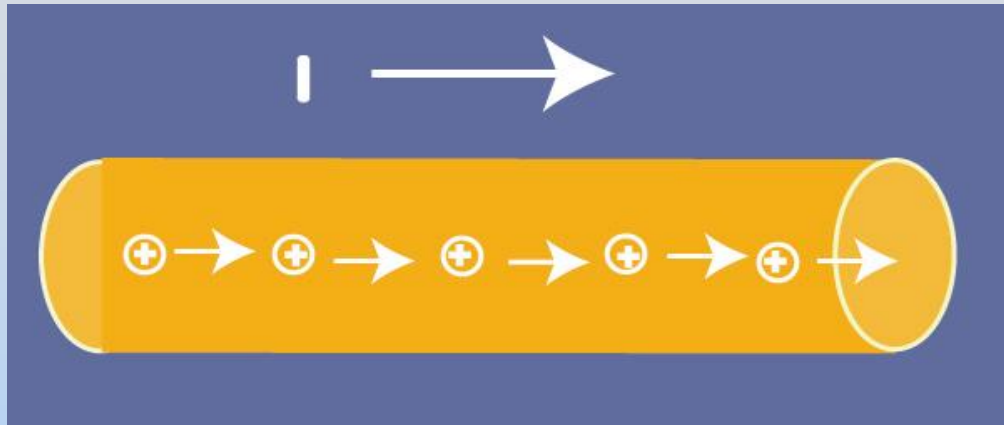
# Direction of The Current

Direction of current is direction of flow of pos. charge



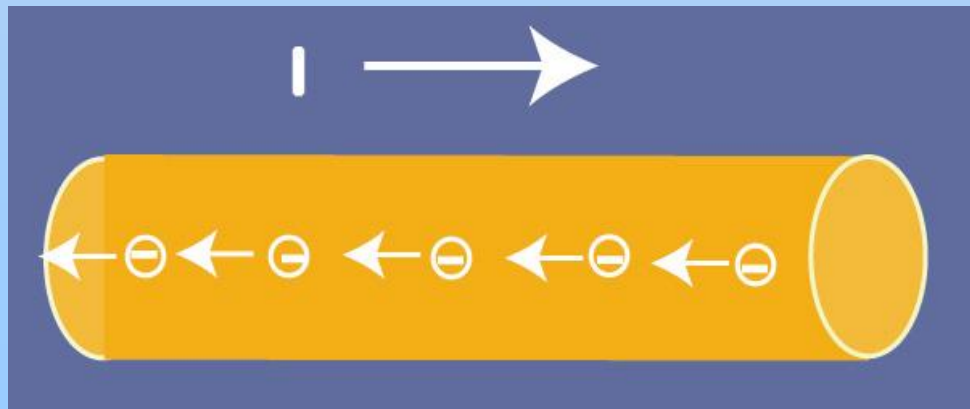or, opposite direction of flow of negative charge




# Current Density $\mathbf{J}$

$\mathbf{J}$ : current/unit area

$$\vec{\mathbf{J}} \equiv \frac{I}{A} \hat{\mathbf{I}}$$

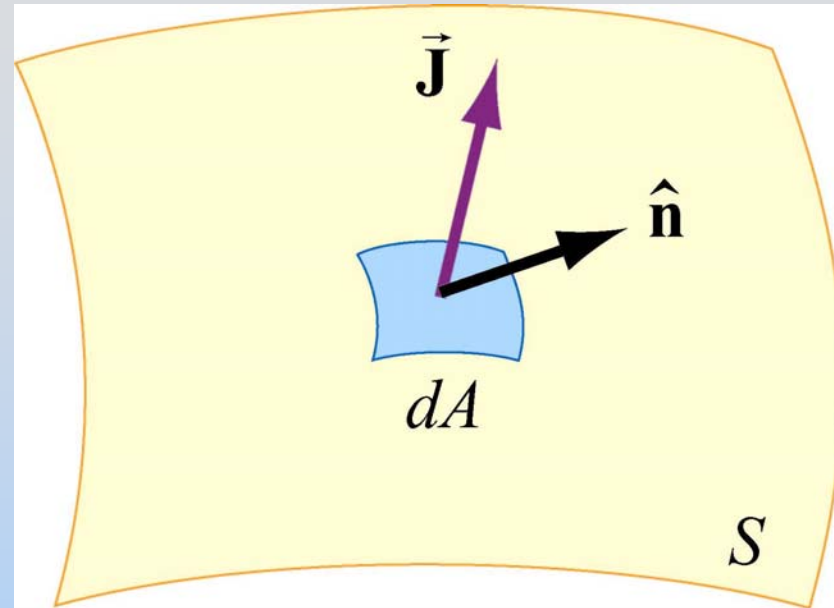$\hat{\mathbf{I}}$  points in direction of current




$$I = \int_S \vec{\mathbf{J}} \cdot \hat{\mathbf{n}} dA = \int_S \vec{\mathbf{J}} \cdot d\vec{\mathbf{A}}$$



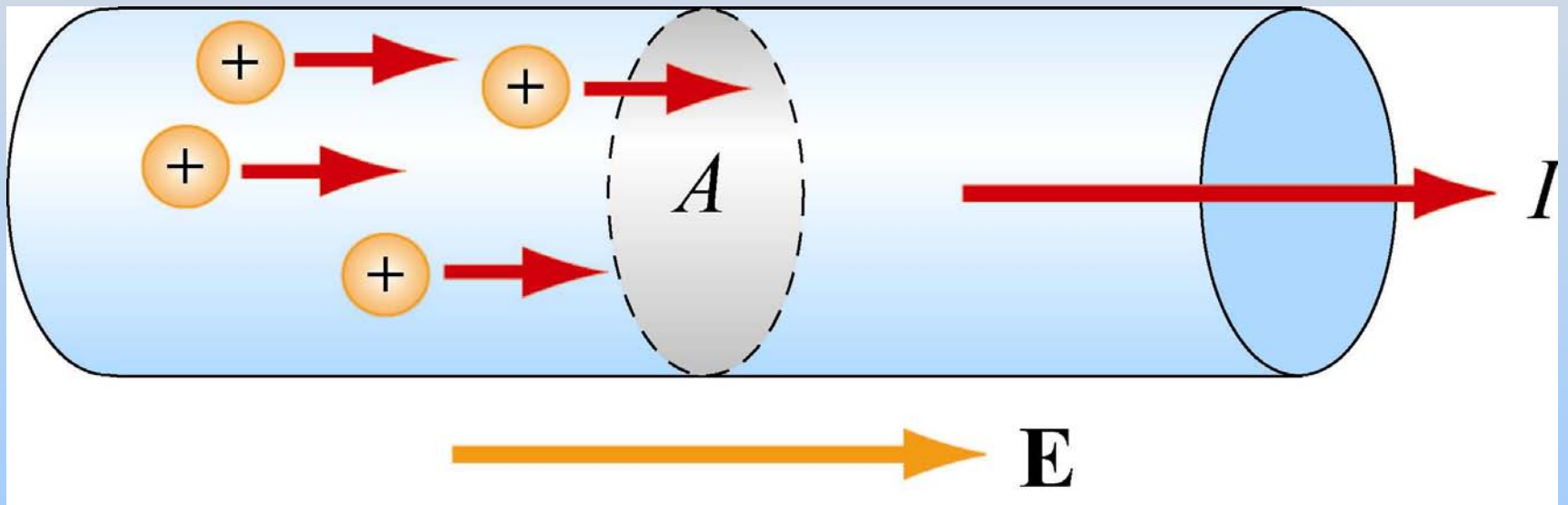
# Why Does Current Flow?

If an electric field is set up in a conductor, charge will move (making a current in direction of  $E$ )



Note that when current is flowing, the conductor is not an equipotential surface (and  $E_{\text{inside}} \neq 0$ )!

# Microscopic Picture

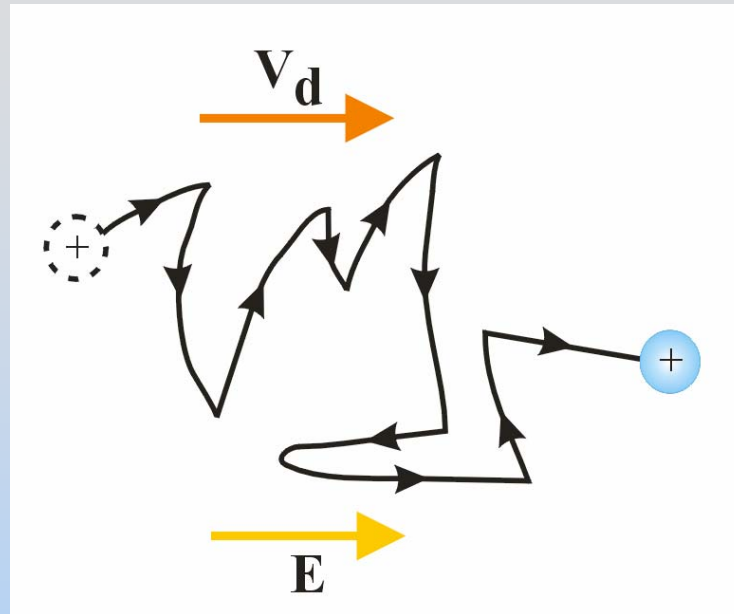


Drift speed is velocity forced by applied electric field in the presence of collisions.

It is typically  $4 \times 10^{-5}$  m/sec, or 0.04 mm/second!

To go one meter at this speed takes about 10 hours!

**How Can This Be?**

# Conductivity and Resistivity

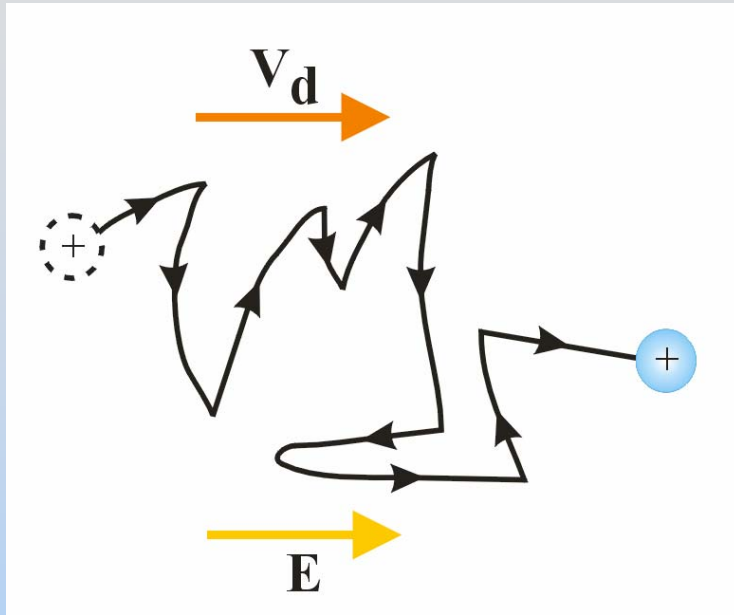

Ability of current to flow depends on density of charges & rate of scattering

Two quantities summarize this:


$\sigma$ : conductivity

$\rho$ : resistivity

# Microscopic Ohm's Law

$$\vec{\mathbf{E}} = \rho \vec{\mathbf{J}} \quad \text{or} \quad \vec{\mathbf{J}} = \sigma \vec{\mathbf{E}}$$

$$\rho \equiv \frac{1}{\sigma}$$

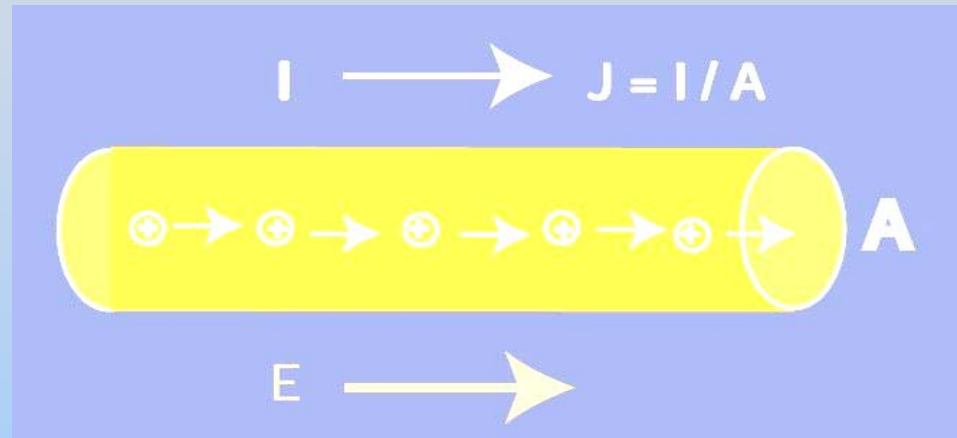


$\rho$  and  $\sigma$  depend only on the microscopic properties of the material, not on its shape

# **Demonstrations: Temperature Effects on $\rho$**

# **PRS Questions: Resistance?**
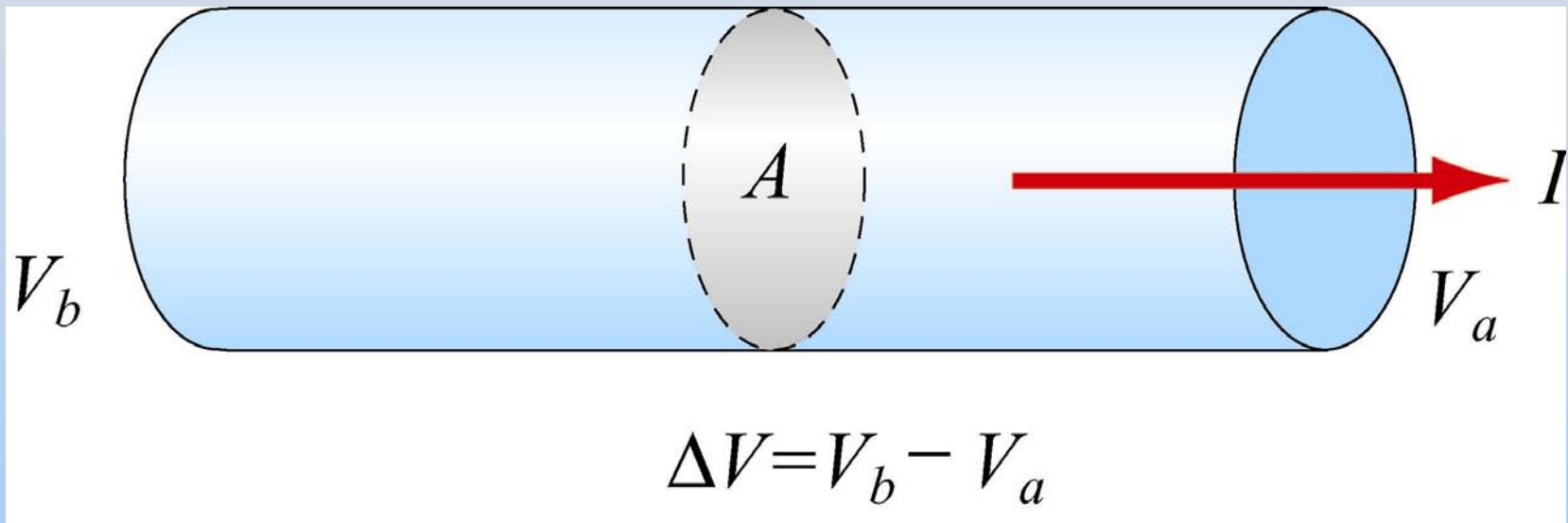
# Why Does Current Flow?


Instead of thinking of Electric Field, think of potential difference across the conductor


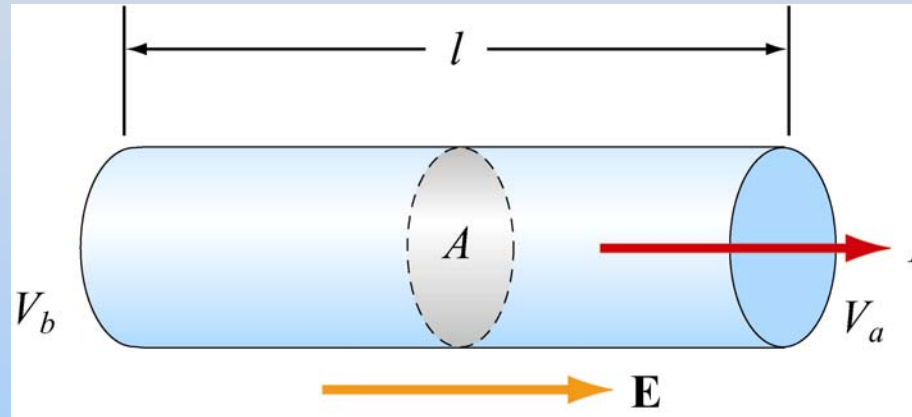
# Ohm's Law

What is relationship between  $\Delta V$  and current?


$$\Delta V = V_b - V_a = -\int_a^b \vec{\mathbf{E}} \cdot d\vec{\mathbf{s}} = E\ell$$



$$\left. \begin{aligned} J &= \frac{E}{\rho} = \frac{\Delta V / \ell}{\rho} \\ J &= \frac{I}{A} \end{aligned} \right\} \Rightarrow \Delta V = I \left( \frac{\rho \ell}{A} \right) \equiv IR$$



# Ohm's Law


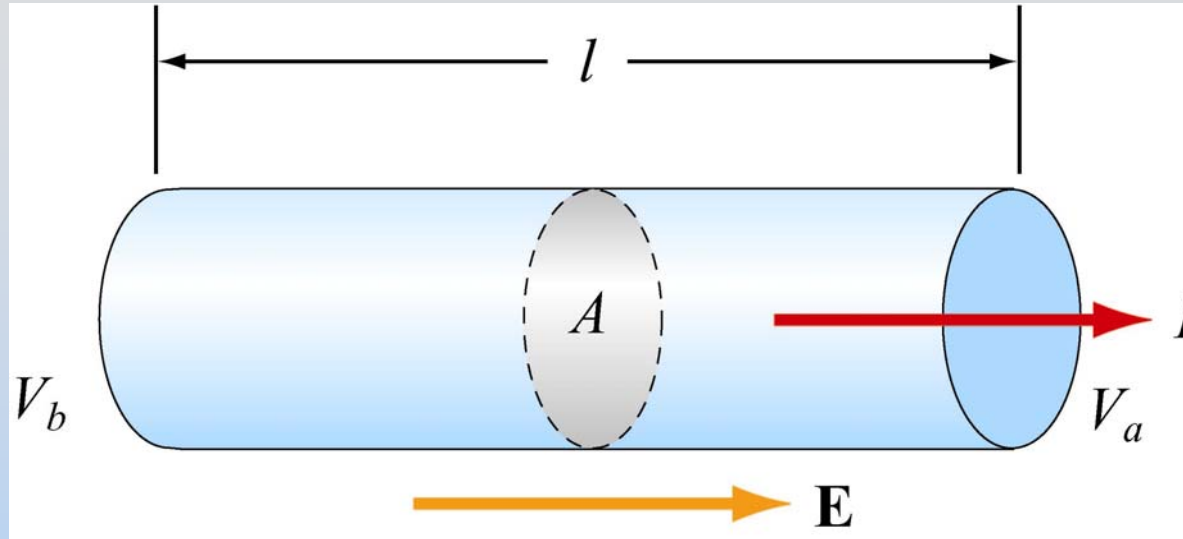


$$\Delta V = IR$$





$$R = \frac{\rho l}{A}$$

R has units of Ohms ( $\Omega$ ) = Volts/Amp
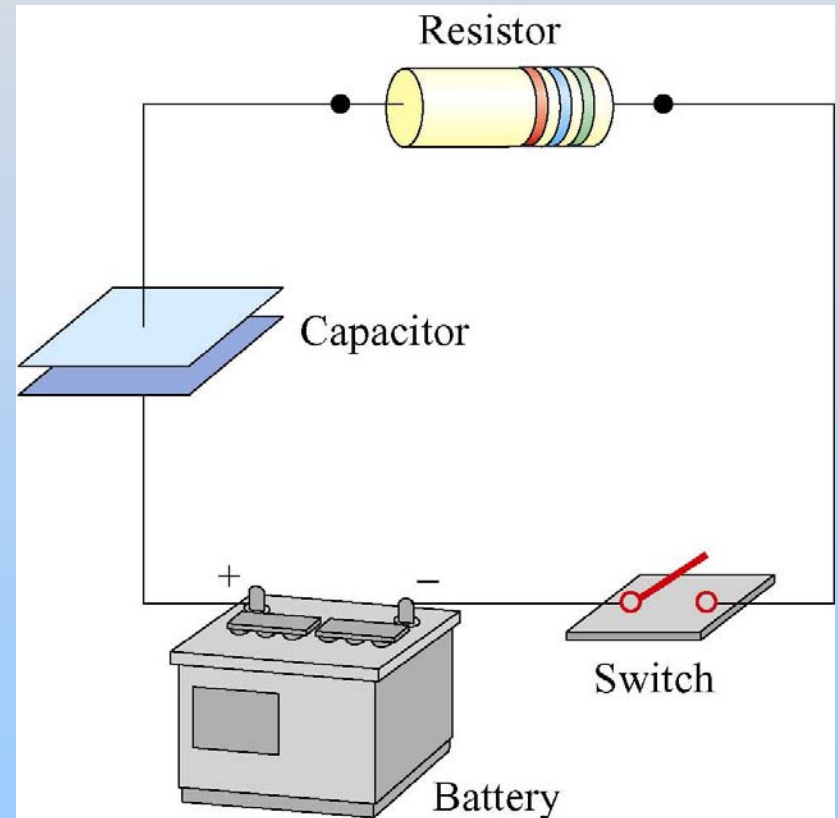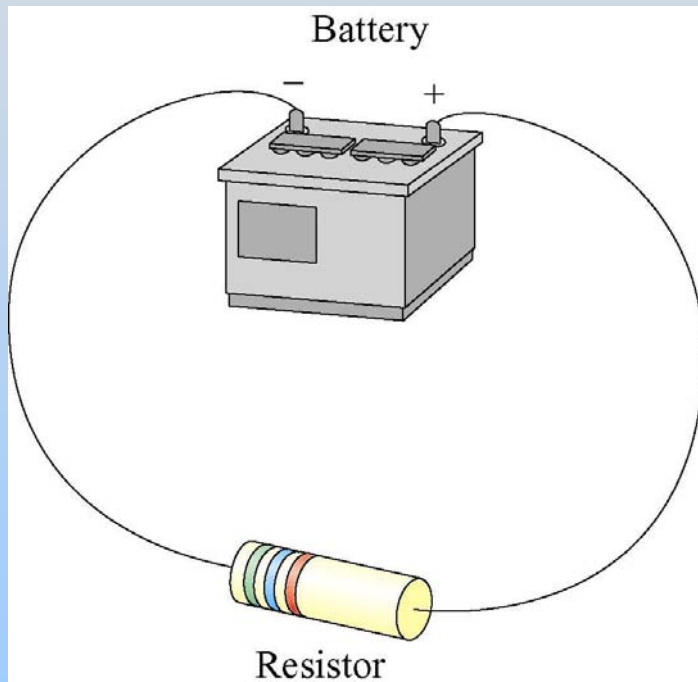
# Examples of Circuits

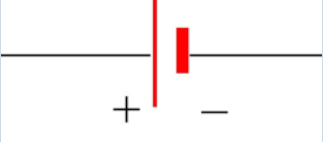


# Symbols for Circuit Elements


<b>Battery</b>	
<b>Resistor</b>	
<b>Capacitor</b>	
<b>Switch</b>	
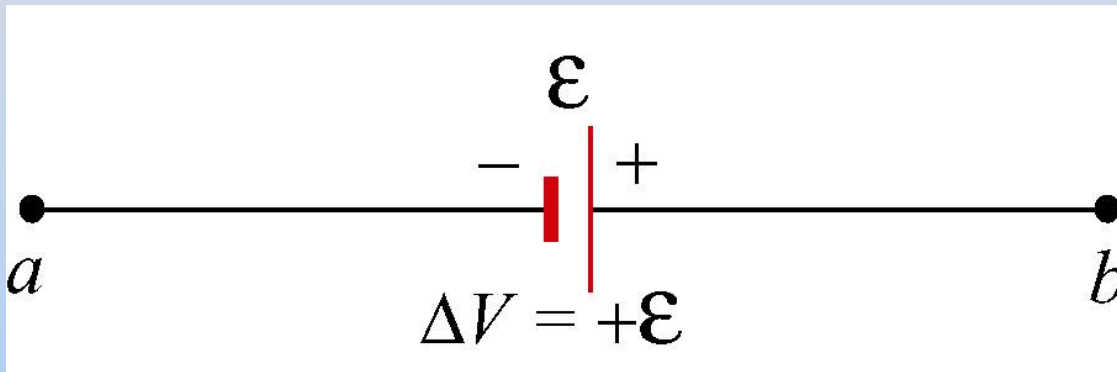
# Sign Conventions - Battery

Moving from the negative to positive terminal of a battery **increases** your potential




$$\Delta V = V_b - V_a$$

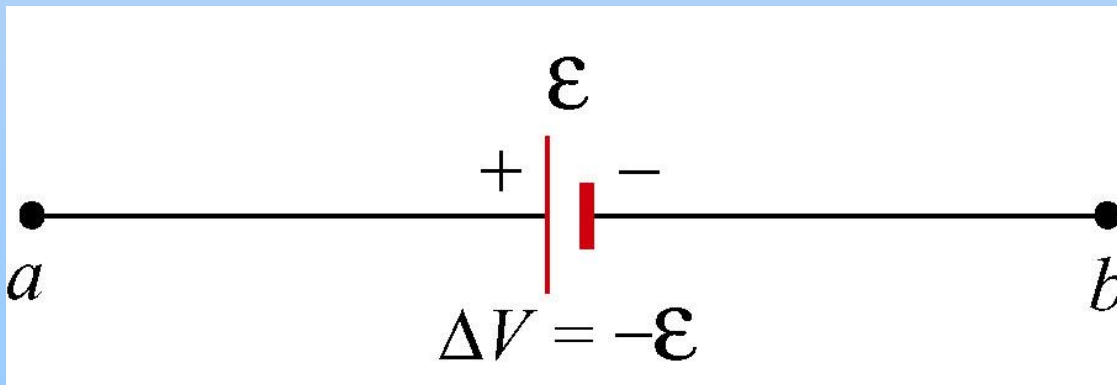


**Think:  
Ski Lift**
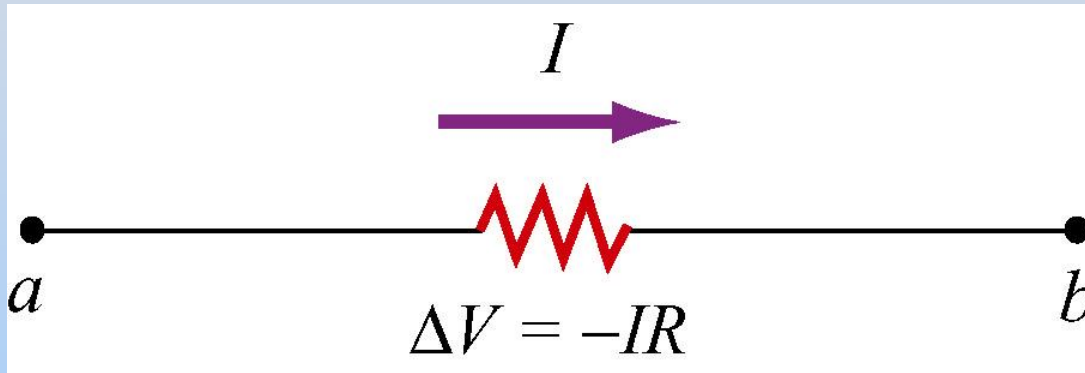
# Sign Conventions - Resistor

Moving across a resistor in the direction of current **decreases** your potential




$$\Delta V = V_b - V_a$$

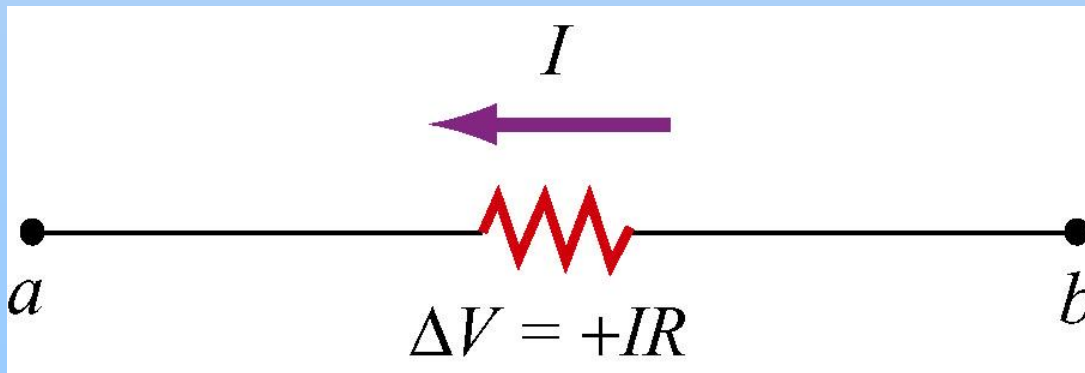


**Think:**  
**Ski Slope**
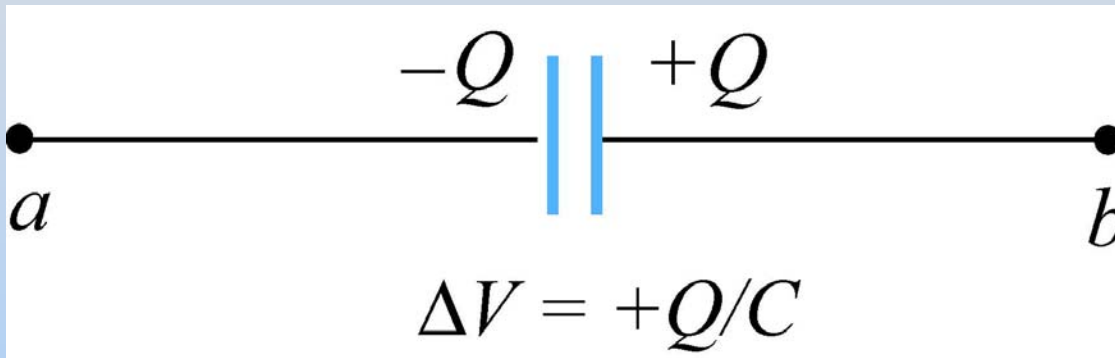
# Sign Conventions - Capacitor

Moving across a capacitor from the negatively to positively charged plate **increases** your potential




$$\Delta V = V_b - V_a$$

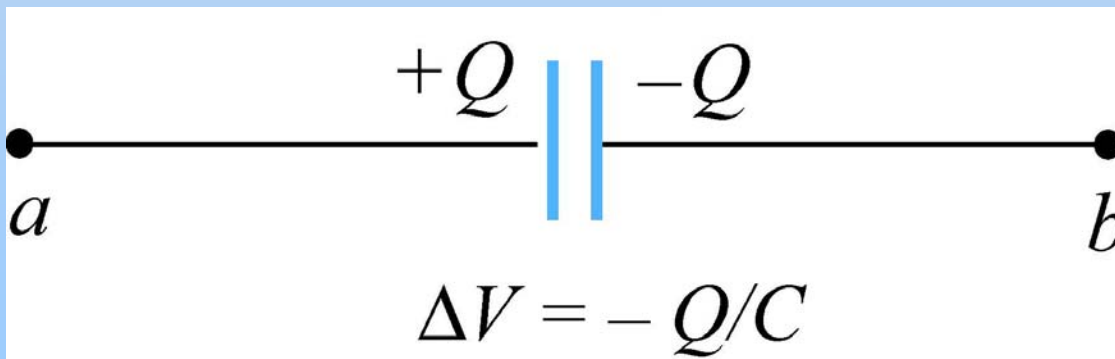


**Think:**  
**Ski Lodge**

# Series vs. Parallel

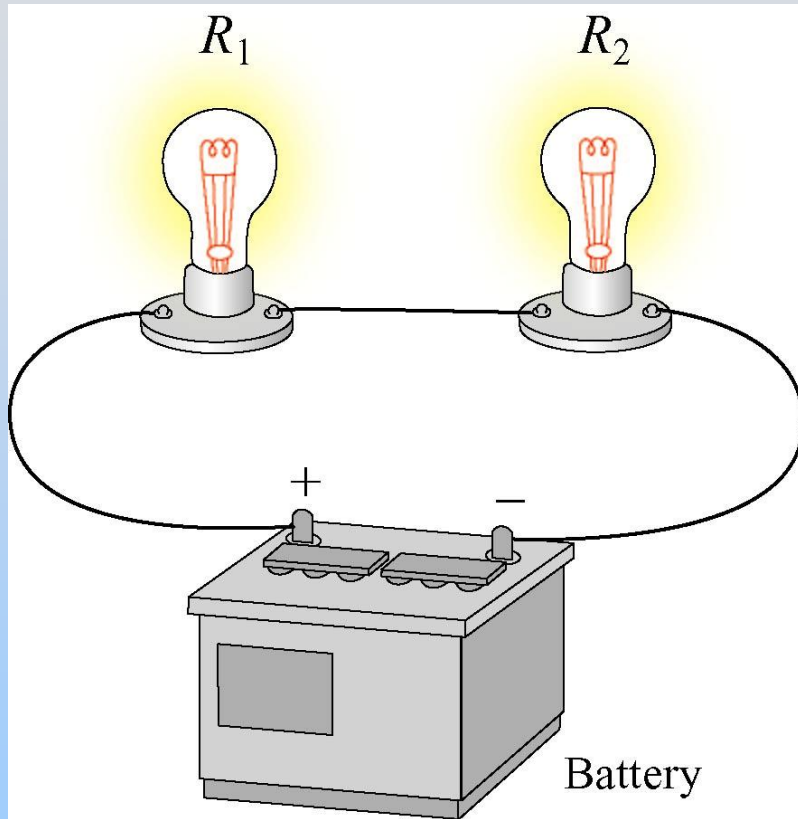



**Series**

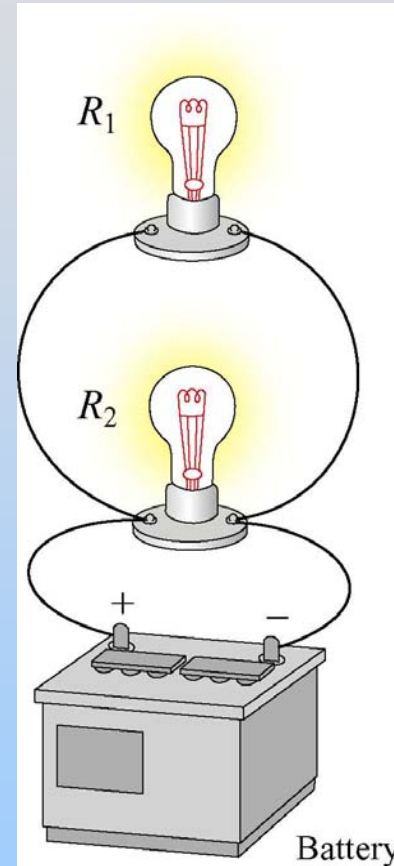

**Parallel**
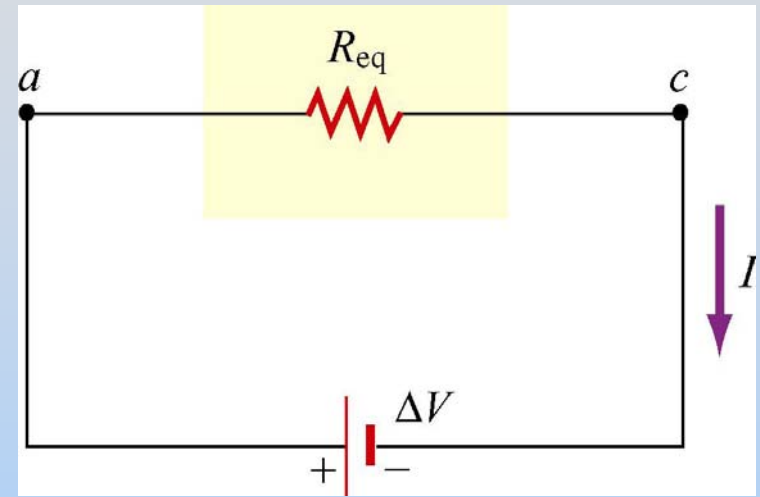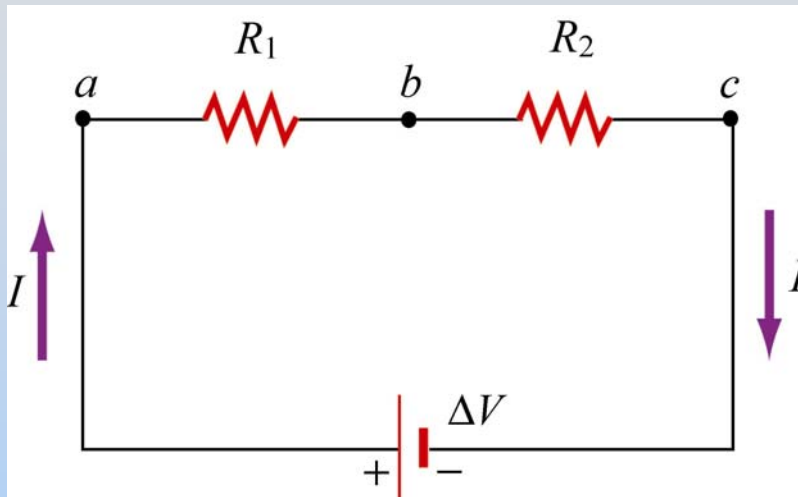
# Resistors In Series

The same current  $I$  must flow through both resistors





$$\Delta V = I R_1 + I R_2 = I(R_1 + R_2) = I R_{eq}$$

$$R_{eq} = R_1 + R_2$$


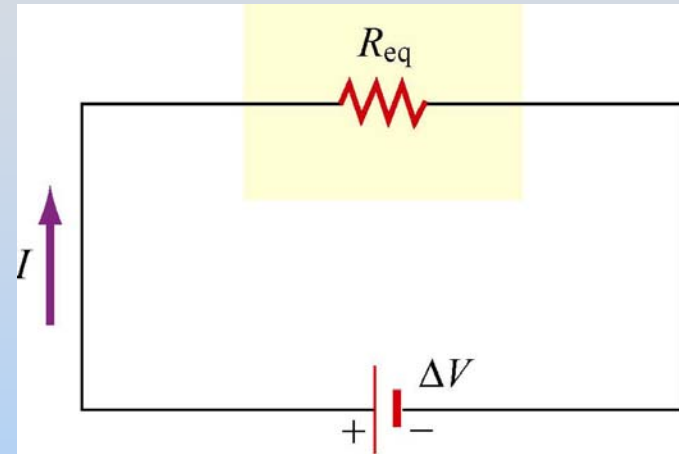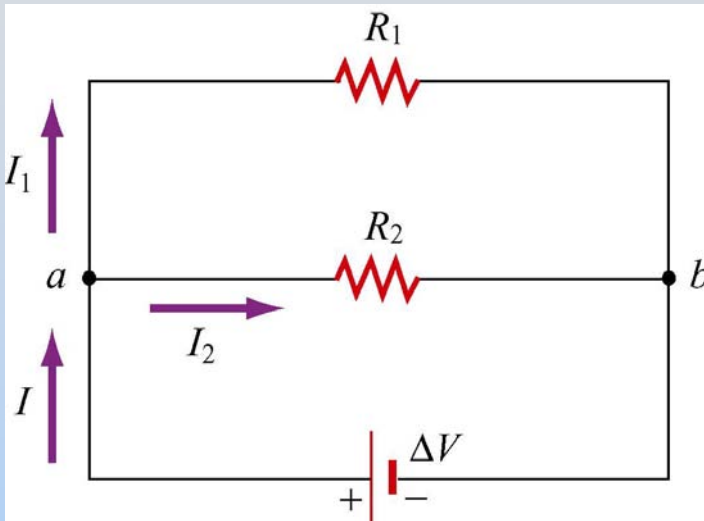
# Resistors In Parallel

Voltage drop across the resistors must be the same



$$\Delta V = \Delta V_1 = \Delta V_2 = I_1 R_1 = I_2 R_2 = I R_{eq}$$

$$I = I_1 + I_2 = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} = \frac{\Delta V}{R_{eq}}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

# **PRS Questions: Light Bulbs**

# Kirchhoff's Loop Rules

# Kirchhoff's Rules

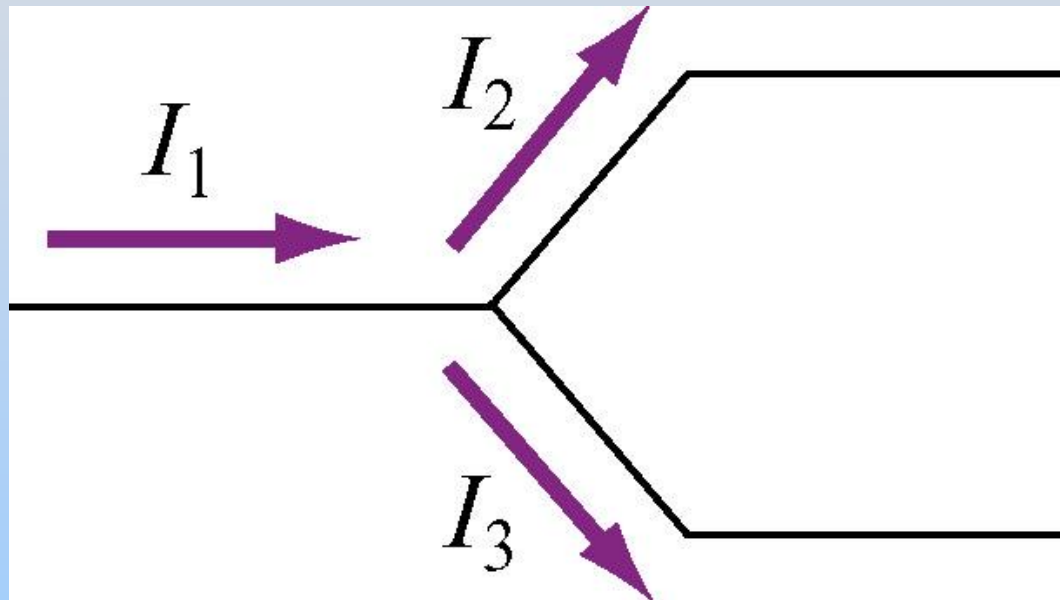1. Sum of currents entering any junction in a circuit must equal sum of currents leaving that junction.





$$I_1 = I_2 + I_3$$
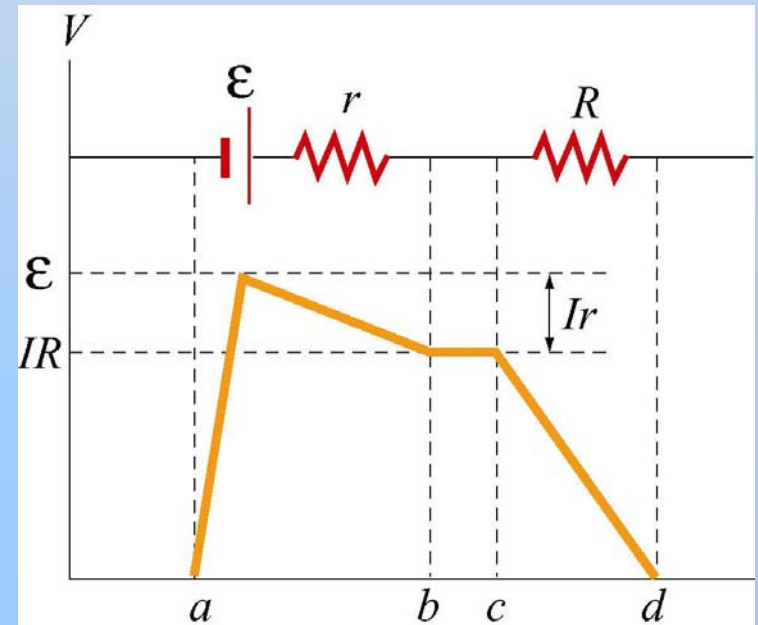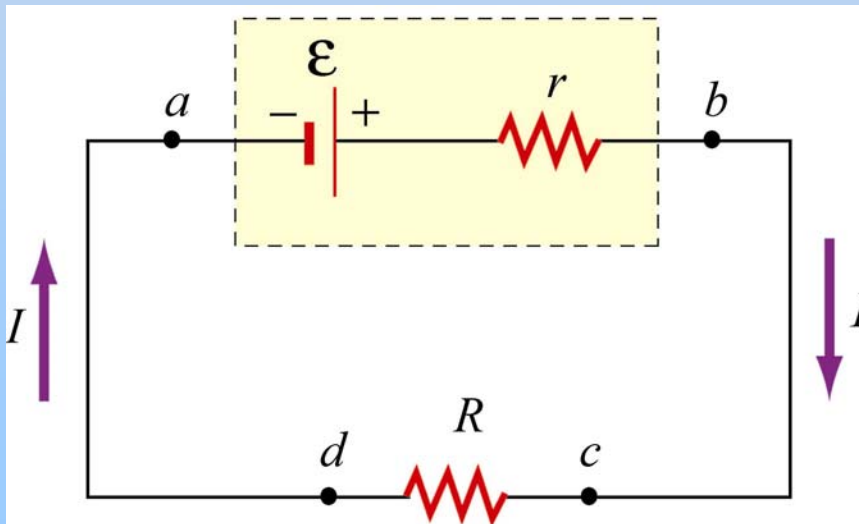
# Kirchhoff's Rules


- Sum of potential differences across all elements around any closed circuit loop must be zero.

$$\Delta V = - \oint_{\text{Closed Path}} \vec{\mathbf{E}} \cdot d\vec{\mathbf{s}} = 0$$


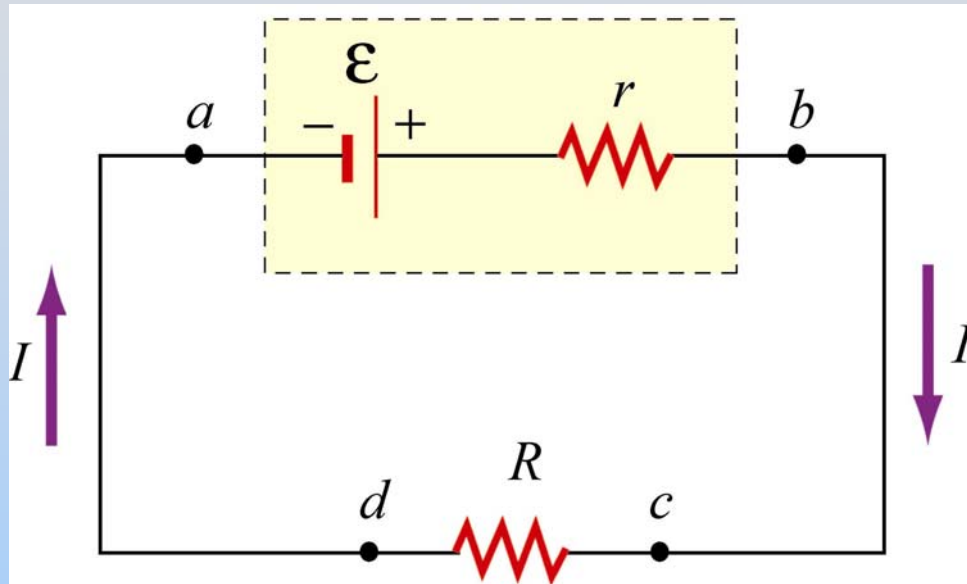
# Internal Resistance

Real batteries have an internal resistance,  $r$ , which is small but non-zero




Terminal voltage:  $\Delta V = V_b - V_a = \mathcal{E} - I r$

(Even if you short the leads you don't get infinite current)

# Steps of Solving Circuit Problem


1. Straighten out circuit (make squares)
2. Simplify resistors in series/parallel
3. Assign current loops (arbitrary)
4. Write loop equations (1 per loop)
5. Solve

# Example: Simple Circuit

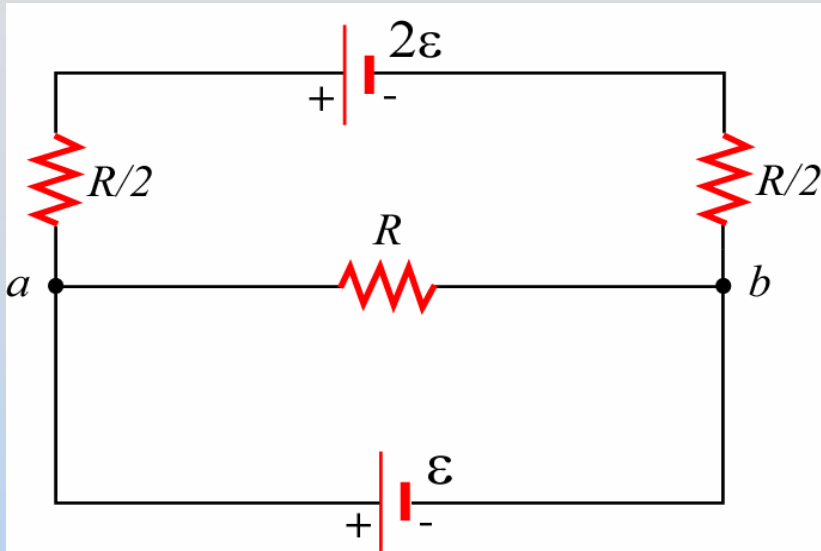


You can simplify resistors in series (but don't need to)

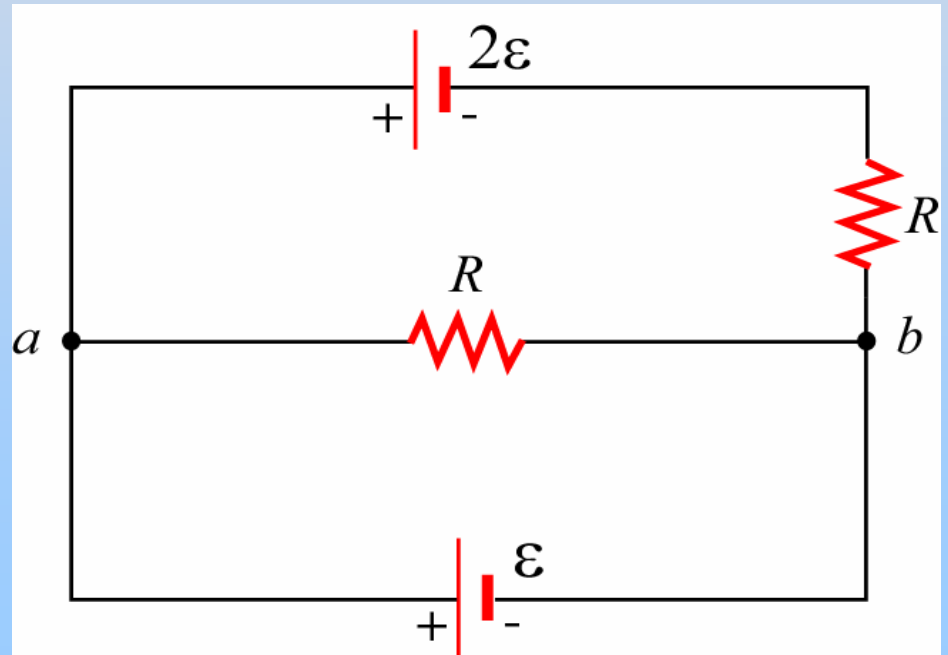What is current through the bottom battery?





# Example: Simple Circuit

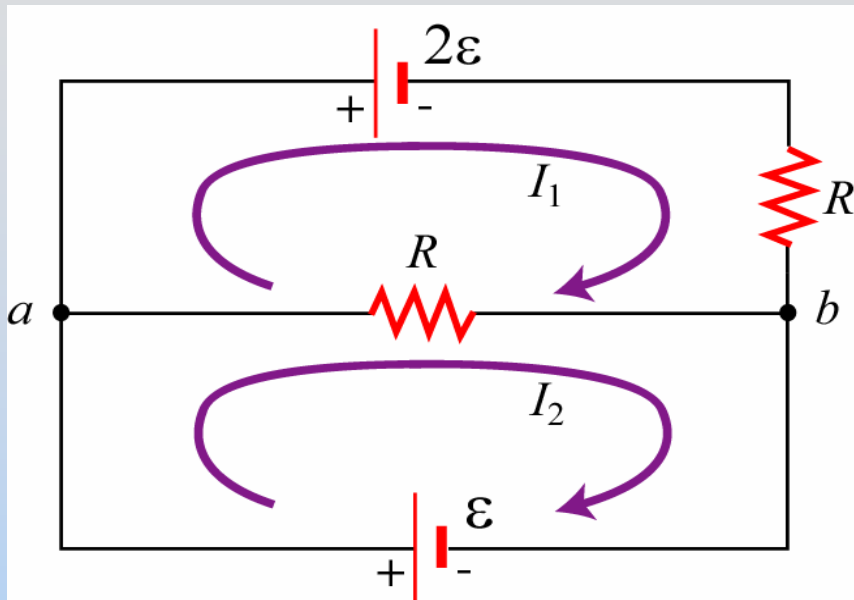

Start at  $a$  in both loops  
Walk in direction of current  
 $-2\varepsilon - I_1 R - (I_1 - I_2) R = 0$

$$-(I_2 - I_1) R + \varepsilon = 0$$


Add these:  $-2\varepsilon - I_1 R + \varepsilon = 0 \rightarrow I_1 = \frac{-\varepsilon}{R}$

We wanted  $I_2$ :  $(I_2 - I_1) R = \varepsilon \rightarrow I_2 = \frac{\varepsilon}{R} + I_1$


$$I_2 = 0$$
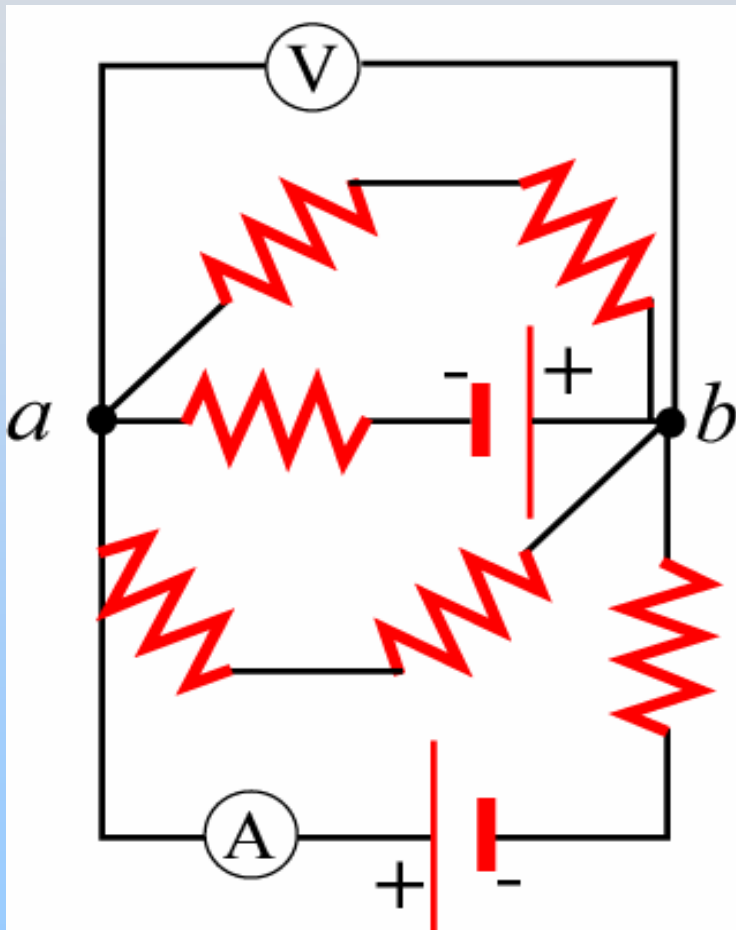
# Group Problem: Circuit

Find meters' values. All resistors are  $R$ , batteries are  $\mathcal{E}$



HARDER

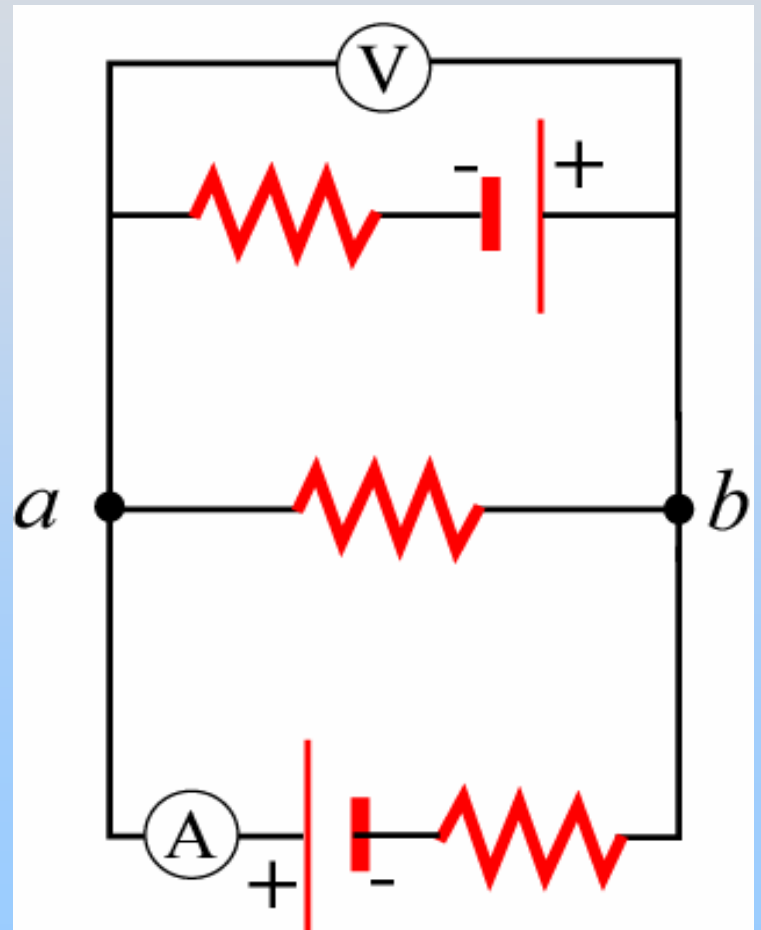

EASIER

# Power

# Electrical Power

Power is change in energy per unit time


So power to move current through circuit elements:

$$P = \frac{d}{dt} U = \frac{d}{dt} (q \Delta V) = \frac{dq}{dt} \Delta V$$

$$P = I \Delta V$$
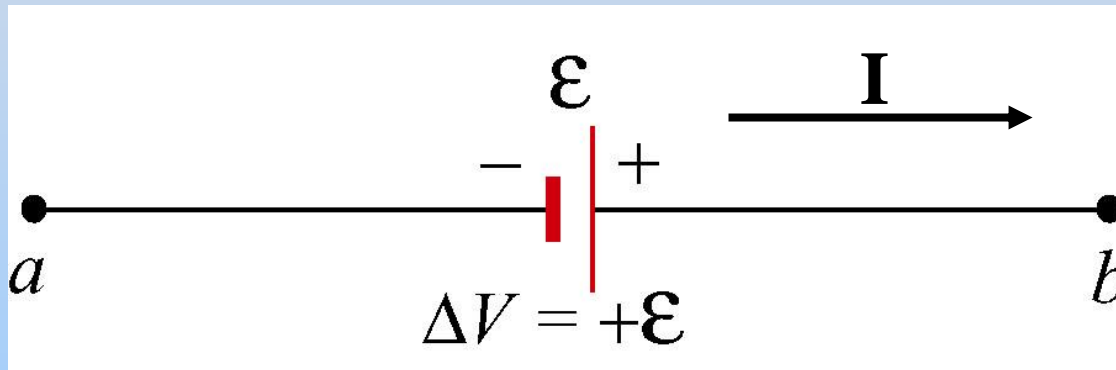
# Power - Battery


Moving from the negative to positive terminal of a battery **increases** your potential. If current flows in that direction the battery **supplies** power



$$P_{\text{supplied}} = I \Delta V = I \epsilon$$
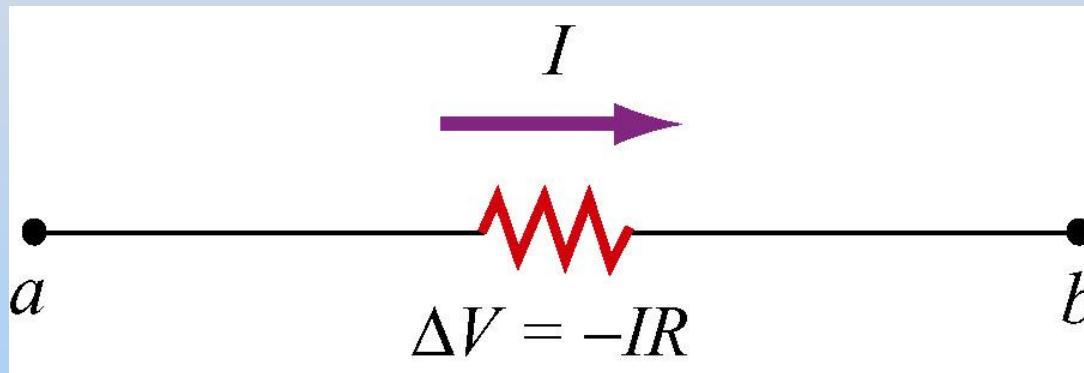
# Power - Resistor


Moving across a resistor in the direction of current **decreases** your potential. Resistors always **dissipate** power



$$P_{\text{dissipated}} = I \Delta V = I^2 R = \frac{\Delta V^2}{R}$$

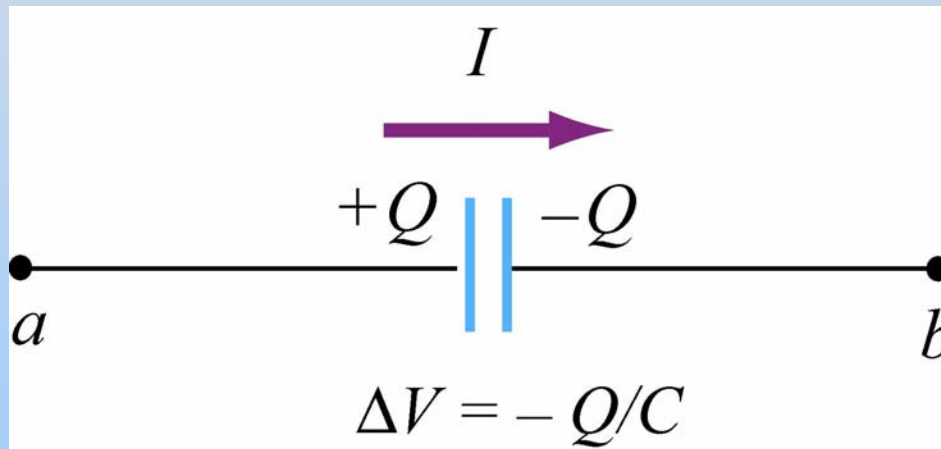
# Power - Capacitor

Moving across a capacitor from the positive to negative plate **decreases** your potential. If current flows in that direction the capacitor **absorbs** power (stores charge)



$$P_{\text{absorbed}} = I \Delta V = \frac{dQ}{dt} \frac{Q}{C} = \frac{d}{dt} \frac{Q^2}{2C} = \frac{dU}{dt}$$

# Energy Balance

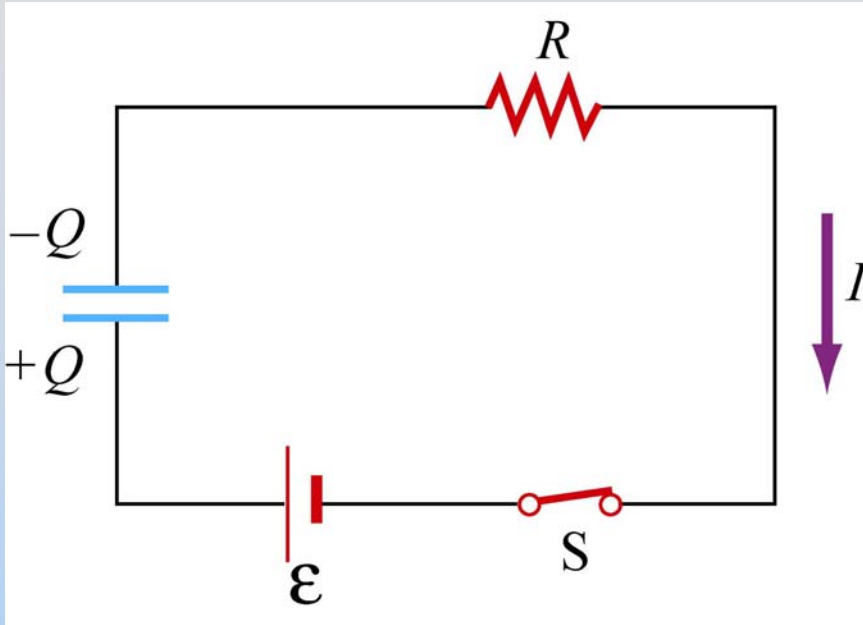

$$\mathcal{E} - \frac{Q}{C} - IR = 0$$

Multiplying by  $I$ :

$$\mathcal{E}I = I^2R + \frac{Q}{C} \frac{dQ}{dt} = I^2R + \frac{d}{dt} \left( \frac{1}{2} \frac{Q^2}{C} \right)$$

(power delivered by battery) = (power dissipated through resistor)  
+ (power absorbed by the capacitor)



# **PRS Questions: More Light Bulbs**