

## DC Circuits Challenge Problem Solutions


### Problem 1:

A battery of emf  $\mathcal{E}$  has internal resistance  $R_i$ , and let us suppose that it can provide the emf to a total charge  $Q$  before it expires. Suppose that it is connected by wires with negligible resistance to an external (load) with resistance  $R_L$ .

- a) What is the current in the circuit?
- b) What value of  $R_L$  maximizes the current extracted from the battery, and how much chemical energy is generated in the battery before it expires?
- c) What value of  $R_L$  maximizes the total power delivered to the load, and how much energy is delivered to the load before it expires? How does this compare to the energy generated in the battery before it expires?
- d) What value for the resistance in the load  $R_L$  would you need if you want to deliver 90% of the chemical energy generated in the battery to the load? What current should flow? How does the power delivered to the load now compare to the maximum power output you found in part c)?

### Problem 1 Solution:

(a)

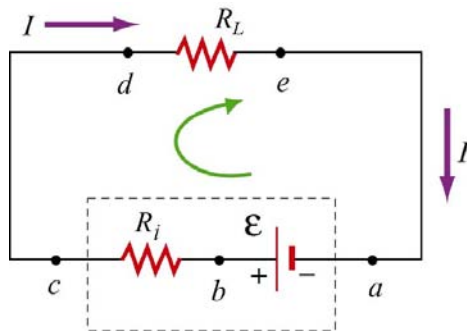

The Kirchoff loop law (the sum of the voltage differences across each element around a closed loop is zero) yields

$$\mathcal{E} - I R_i - I R_L = 0.$$

Solving for the current we find that

$$I = \frac{\mathcal{E}}{R_i + R_L}.$$

(b) The current is maximized when  $R_L = 0$ .

The chemical energy generated in the battery is given by

$$U_{emf} = \int_0^{\Delta t} \mathcal{E} I dt = \mathcal{E} I \Delta t$$

During this time interval, the battery delivers a charge

$$Q = \int_0^{\Delta t} I dt = I \Delta t.$$

Therefore the chemical energy generated is

$$U_{emf} = \mathcal{E} I \Delta t = \mathcal{E} I \frac{Q}{I} = \mathcal{E} Q$$

This result is independent of the current and only depends on the charge  $Q$  that is transferred across the EMF. So for all the following parts, this quantity is the same.

All of this chemical energy is dissipated into thermal energy due to the internal resistance of the battery to the flow of current. When the battery stops delivering current, the battery will reach thermal equilibrium with the surroundings and this thermal energy will flow into the surroundings.

(c) The power delivered to the load is

$$P_L = I^2 R_L = \left( \frac{\mathcal{E}}{R_i + R_L} \right)^2 R_L.$$

We can maximize this by considered the derivative with respect to  $R_L$  :

$$\frac{dP_L}{dR_L} = \mathcal{E}^2 \left( \left( \frac{1}{R_i + R_L} \right)^2 - 2R_L \left( \frac{1}{R_i + R_L} \right)^3 \right) = 0.$$

Solve this equation for  $R_L$  :

$$\left(\frac{1}{R_i + R_L}\right)^2 = 2R_L \left(\frac{1}{R_i + R_L}\right)^3,$$

$$R_i + R_L = 2R_L,$$

$$R_L = R_i.$$

The current is then

$$I = \frac{\mathcal{E}}{R_i + R_L} = \frac{\mathcal{E}}{2R_i}.$$

The power delivered to the load is

$$P_{L,\max} = I^2 R_L = \left(\frac{\mathcal{E}}{2R_i}\right)^2 R_i = \frac{1}{4} \frac{\mathcal{E}^2}{R_i}$$

The energy delivered to the load is then

$$U_L = I R_L Q = \frac{\mathcal{E}}{2R_i} R_i Q = \frac{\mathcal{E}Q}{2} = \frac{1}{2} U_{chem}.$$

So exactly half the chemical energy is delivered to the load.

(d) Even though we maximized the power delivered to the load in part (c), we are wasting one half the chemical energy. Suppose you want to waste only 10% of the chemical energy. What current should flow?

$$U_L = 0.9 U_{chem} = 0.9 \mathcal{E}Q = I' R_L Q.$$

This implies that

$$I' R_L = \frac{\mathcal{E}}{R_i + R_L} R_L = 0.9 \mathcal{E}.$$

This is satisfied when

$$R_L = 9R_i.$$

So the current is

$$I' = \frac{\mathcal{E}}{10R_i} .$$

The power output is then

$$P_L = I'^2 R_L = \left( \frac{\mathcal{E}}{10R_i} \right)^2 9R_i = \frac{9}{25} \left( \frac{1}{4} \frac{\mathcal{E}^2}{R_i} \right) = \frac{9}{25} P_{L,\max} .$$

So we waste 10% of the energy and still maintain 36% of the maximum power output.

## Problem 2:

AAA, AA, ... D batteries have an open circuit voltage (EMF) of 1.5 V. The difference between different sizes is in their lifetime (total energy storage). A AAA battery has a life of about 0.5 A-hr while a D battery has a life of about 10 A-hr. Of course these numbers depend on how quickly you discharge them and on the manufacturer, but these numbers are roughly correct. One important difference between batteries is their internal resistance – alkaline (now the standard) D cells are about  $0.1\Omega$ .

Suppose that you have a multi-speed winch that is 50% efficient (50% of energy used does useful work) run off a D cell, and that you are trying to lift a mass of 60 kg (hmmm, I wonder what mass that would be). The winch acts as load with a variable resistance  $R_L$  that is speed dependent.

- Suppose the winch is set to super-slow speed. Then the load (winch motor) resistance is much greater than the battery's internal resistance and you can assume that there is no loss of energy to internal resistance. How high can the winch lift the mass before discharging the battery?
- To what resistance  $R_L$  should the winch be set in order to have the battery lift the mass at the fastest rate? What is this fastest rate (m/sec)? HINT: You want to maximize the power delivery to the winch (power dissipated by  $R_L$ ).
- At this fastest lift rate how high can the winch lift the mass before discharging the battery?
- Compare the cost of powering a desk light with D cells as opposed to plugging it into the wall. Does it make sense to use rechargeable batteries? Residential electricity costs about \$0.1/kwh.

## Problem 2 Solutions:

(a) This is just a question of energy. The battery has an energy storage of  $(1.5\text{ V})(10\text{ A-hr}) = 15\text{ W-hr}$  or 54 kJ. So it can lift the mass:

$$U = mgh \Rightarrow h = \frac{U}{mg} = \frac{54\text{ kJ} \cdot \frac{1}{2}}{(60\text{ kg})(9.8\text{ m/s}^2)} = \boxed{46\text{ m}}$$

The factor of a half is there because the winch is only 50% efficient.

(b) First we need to determine how to maximize power delivery. If a battery  $V$  is connected to two resistances,  $r_i$  (the internal resistance) and  $R$ , the load resistance, the power dissipated in the load is:

$$P = I^2 R = \left( \frac{V_0}{R + r_i} \right)^2 R = V_0^2 \frac{R}{(R + r_i)^2}$$

We want to maximize this by varying  $R$ :

$$\frac{dP}{dR} = \frac{d}{dR} \left( V_0^2 R (R + r_i)^{-2} \right) = V_0^2 \left[ (R + r_i)^{-2} - 2R (R + r_i)^{-3} \right] = 0$$

Multiply both sides by  $V_0^{-2} (R + r_i)^3$  :  $[(R + r_i) - 2R] = r_i - R = 0 \Rightarrow \boxed{R = r_i}$

So, to get the fastest rate of lift (most power dissipation in the winch) we need the winch resistance to equal the battery internal resistance,  $R_L = r_i = 0.1 \Omega$ .

Using this we can get the lift rate from the power:

$$P = I^2 R_L = \left( \frac{V_0}{R_L + r_i} \right)^2 R_L = \frac{V_0^2}{4r_i} \stackrel{50\% \text{ eff}}{\approx} \frac{d}{dt} (mgh) \Rightarrow v = \frac{dh}{dt} = \frac{V_0^2}{8r_i mg}$$

Thus we find a lift rate of  $\boxed{v = 4.8 \text{ mm/s}}$

(c) This is just part a over again, except now we waste half the energy in the internal resistor, so the winch will only rise half as high, to  $\boxed{23 \text{ m}}$


d)

A D cell has a battery life of 10 A-hr, meaning a total energy storage of  $(1.5 \text{ V})(10 \text{ A-hr}) = 15 \text{ Watt-hrs}$ . We could convert that to about 50 kJ but Watt-hours are a useful unit to use because electricity is typically charged by the kW-hour so this will make comparison easier. A D battery costs about \$1 (you can pay more, but why?) So D batteries cost about \$1/0.015 kWh or \$70/kWh.

Residential electricity costs about \$0.1/kWh. So the battery is nearly three orders of magnitude more expensive. It definitely makes sense to use rechargeable batteries – even though the upfront cost is slightly more expensive you will get it back in a couple recharges. As for your desk light, or anything that can run on batteries or wall power, plug it in. If it is 60 Watts, for every hour you pay only 0.6¢ with wall power but run through \$4 in D batteries.
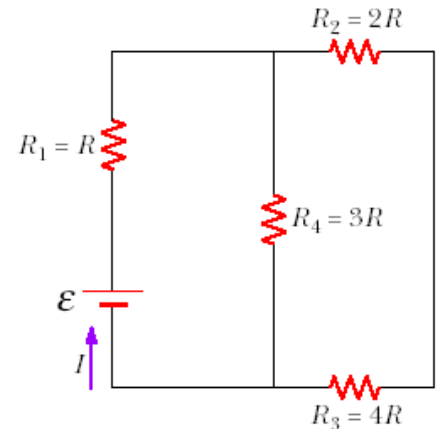
### Problem 3:

Four resistors are connected to a battery as shown in the figure. The current in the battery is  $I$ , the battery emf is  $\mathcal{E}$ , and the resistor values are  $R_1 = R$ ,  $R_2 = 2R$ ,  $R_3 = 4R$ ,  $R_4 = 3R$ .



(a) Rank the resistors according to the potential difference across them, from largest to smallest. Note any cases of equal potential differences.

(b) Determine the potential difference across each resistor in terms of  $\mathcal{E}$ .

(c) Rank the resistors according to the current in them, from largest to smallest. Note any cases of equal currents.

(d) Determine the current in each resistor in terms of  $I$ .

(e) If  $R_3$  is increased, what happens to the current in each of the resistors?

(f) In the limit that  $R_3 \rightarrow \infty$ , what are the new values of the current in each resistor in terms of  $I$ , the original current in the battery?

### Problem 3 Solutions:

(a) Resistors 2 and 3 can be combined (in series) to give  $R_{23} = R_2 + R_3 = 2R + 4R = 6R$ .

$R_{23}$  is in parallel with  $R_4$  and the equivalent resistance  $R_{234}$  is

$$R_{234} = \frac{R_{23}R_4}{R_{23} + R_4} = \frac{(6R)(3R)}{6R + 3R} = 2R$$

Since  $R_{234}$  is in series with  $R_1$ , the equivalent resistance of the whole circuit is

$R_{1234} = R_1 + R_{234} = R + 2R = 3R$ . In series, potential difference is shared in proportion to the resistance, so  $R_1$  gets  $1/3$  of the battery voltage ( $\Delta V_1 = \mathcal{E}/3$ ) and  $R_{234}$  gets  $2/3$  of the battery voltage ( $\Delta V_{234} = 2\mathcal{E}/3$ ). This is the potential difference across  $R_4$  ( $\Delta V_4 = 2\mathcal{E}/3$ ), but  $R_2$  and  $R_3$  must share this voltage:  $1/3$  goes to  $R_2$  ( $\Delta V_2 = (1/3)(2\mathcal{E}/3) = 2\mathcal{E}/9$ ) and  $2/3$  to  $R_3$  ( $\Delta V_3 = (2/3)(2\mathcal{E}/3) = 4\mathcal{E}/9$ ). The ranking by potential difference is  $\Delta V_4 > \Delta V_3 > \Delta V_1 > \Delta V_2$ .

(b) As shown from the reasoning above, the potential differences are

$$\Delta V_1 = \frac{\varepsilon}{3}, \quad \Delta V_2 = \frac{2\varepsilon}{9}, \quad \Delta V_3 = \frac{4\varepsilon}{9}, \quad \Delta V_4 = \frac{2\varepsilon}{3}$$

(c) All the current goes through  $R_1$ , so it gets the most ( $I_1 = I$ ). The current then splits at the parallel combination.  $R_4$  gets more than half, because the resistance in that branch is less than in the other branch.  $R_2$  and  $R_3$  have equal currents because they are in series. The ranking by current is  $I_1 > I_4 > I_2 = I_3$ .

(d)  $R_1$  has a current of  $I$ . Because the resistance of  $R_2$  and  $R_3$  in series ( $R_{23} = R_2 + R_3 = 2R + 4R = 6R$ ) is twice that of  $R_4 = 3R$ , twice as much current goes through  $R_4$  as through  $R_2$  and  $R_3$ . The current through the resistors are

$$I_1 = I, \quad I_2 = I_3 = \frac{I}{3}, \quad I_4 = \frac{2I}{3}$$

(e) Since

$$R_{1234} = R_1 + R_{234} = R_1 + \frac{R_{23}R_4}{R_{23} + R_4} = R_1 + \frac{(R_2 + R_3)R_4}{R_2 + R_3 + R_4}$$

increasing  $R_3$  increases the equivalent resistance of the entire circuit. The current in the circuit, which is the current through  $R_1$ , decreases. This decreases the potential difference across  $R_1$ , increasing the potential difference across the parallel combination. With a larger potential difference the current through  $R_4$  is increased. With more current going through  $R_4$ , and less in the circuit to start with, the current through  $R_2$  and  $R_3$  must decrease. Thus,

$I_4$  increases and  $I_1$ ,  $I_2$ , and  $I_3$  decrease

(f) If  $R_3$  has an infinite resistance, it blocks any current from passing through that branch and the circuit effectively is just  $R_1$  and  $R_4$  in series with the battery. The circuit now has an equivalent resistance of  $R_{14} = R_1 + R_4 = R + 3R = 4R$ . The current in the circuit drops to  $3/4$  of the original current because the resistance has increased by  $4/3$ . All this current passes through  $R_1$  and  $R_4$ , and none passes through  $R_2$  and  $R_3$ . Therefore,

$$I_1 = \frac{3I}{4}, \quad I_2 = I_3 = 0, \quad I_4 = \frac{3I}{4}$$




**Problem 4:**

In the circuit below, you can neglect the internal resistance of all batteries.

(a) Calculate the current through each battery

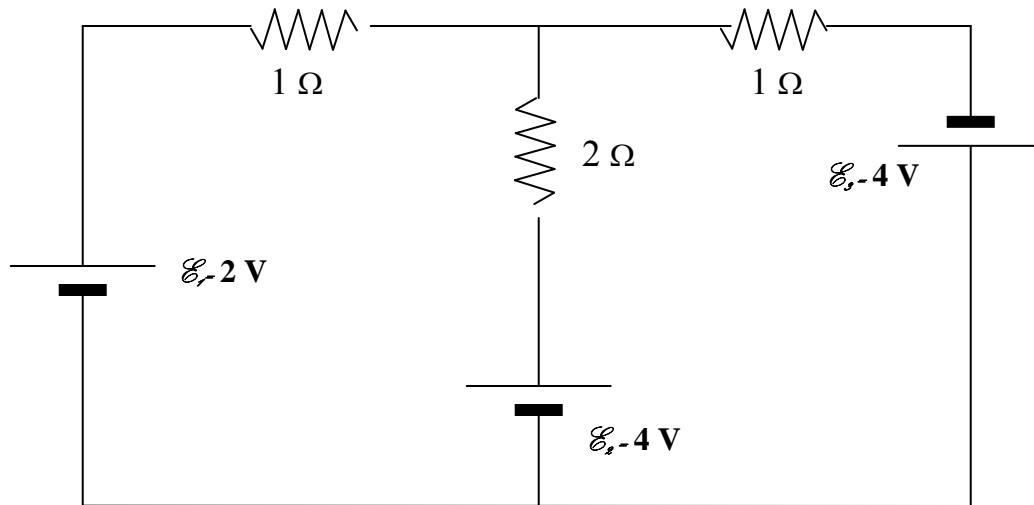
(b) Calculate the power delivered or used (specify which case) by each battery



**Problem 4 Solutions:**

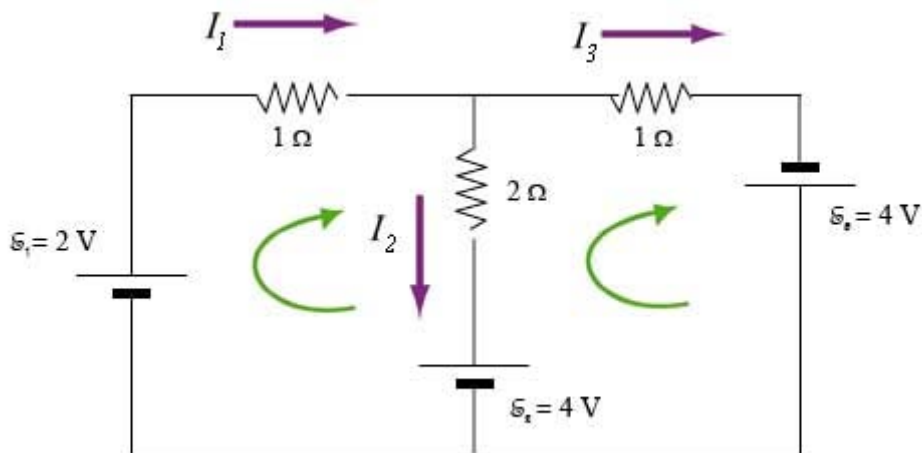(a) Calculate the current through each battery.

We begin by choosing currents in every branch and travel directions in the two loops as shown below.



Current conservation is given by the condition that the current into a junction of branches is equal to the current that leaves that junction:

$$I_1 = I_2 + I_3.$$

The two loop laws for the voltage differences are:

$$2 \text{ V} - (I_1)(1 \Omega) - (I_2)(2 \Omega) - 4 \text{ V} = 0.$$

$$-(I_3)(1 \Omega) + 4 \text{ V} + 4 \text{ V} + (I_2)(2 \Omega) = 0.$$

Strategy: Solve the first loop law for  $I_1$  in terms of  $I_2$ . Solve the second loop law for  $I_3$  in terms of  $I_2$ . Then substitute these results into the current conservation and solve for  $I_2$ . Then determine  $I_1$  and  $I_3$ .

The first loop law becomes

$$I_1 = -2 \text{ A} - 2I_2.$$

The second loop law becomes

$$I_3 = 8 \text{ A} + 2I_2.$$

Current conservation becomes

$$-2 \text{ A} - 2I_2 = I_2 + 8 \text{ A} + 2I_2.$$

Solve for  $I_2$ :

$$I_2 = -2 \text{ A}.$$

Note that the negative sign means the  $I_2$  is flowing in a direction opposite the direction indicated by the arrow. This means that battery 2 is supplying current.

Solve for  $I_1$ :

$$I_1 = -2 \text{ A} - 2(-2 \text{ A}) = 2 \text{ A}$$

Solve for  $I_3$ :

$$I_3 = 8 \text{ A} + 2(-2 \text{ A}) = 4 \text{ A}.$$

(b) Calculate the power delivered or used (specify which case) by each battery.

The power delivered by battery 1 is  $P_1 = (\mathcal{E}_1)(I_1) = (2 \text{ V})(2 \text{ A}) = 4 \text{ W}$ .

The power delivered by battery 2 is  $P_2 = (\mathcal{E}_2)(I_2) = (4 \text{ V})(2 \text{ A}) = 8 \text{ W}$ .

The power delivered by battery 3 is  $P_3 = (\mathcal{E}_3)(I_3) = (4 \text{ V})(4 \text{ A}) = 16 \text{ W}$ .

The total power delivered by the batteries is 28 W

Check: The power delivered to the resistors:

The power delivered to resistor 1 (in left branch)  $P_1 = (I_1^2)(R_1) = (2 \text{ A})^2(1 \Omega) = 4 \text{ W}$  .

The power delivered to resistor 2 (in center branch)  $P_2 = (I_2^2)(R_2) = (2 \text{ A})^2(2 \Omega) = 8 \text{ W}$  .

The power delivered to resistor 3 (in right branch)  $P_3 = (I_3^2)(R_3) = (4 \text{ A})^2(1 \Omega) = 16 \text{ W}$  .

The total power delivered to the resistors is also  $28 \text{ W}$  .

MIT OpenCourseWare  
<http://ocw.mit.edu>

8.02SC Physics II: Electricity and Magnetism  
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.